

LVC MOS Terminations

Figure 1. LVC MOS Series Termination

 


Figure 2. LVC MOS to 2.5V LVC MOS

 


Figure 3. LVC MOS to 1.8V

 


Figure 4. LVCMOS Signal to Differential Input



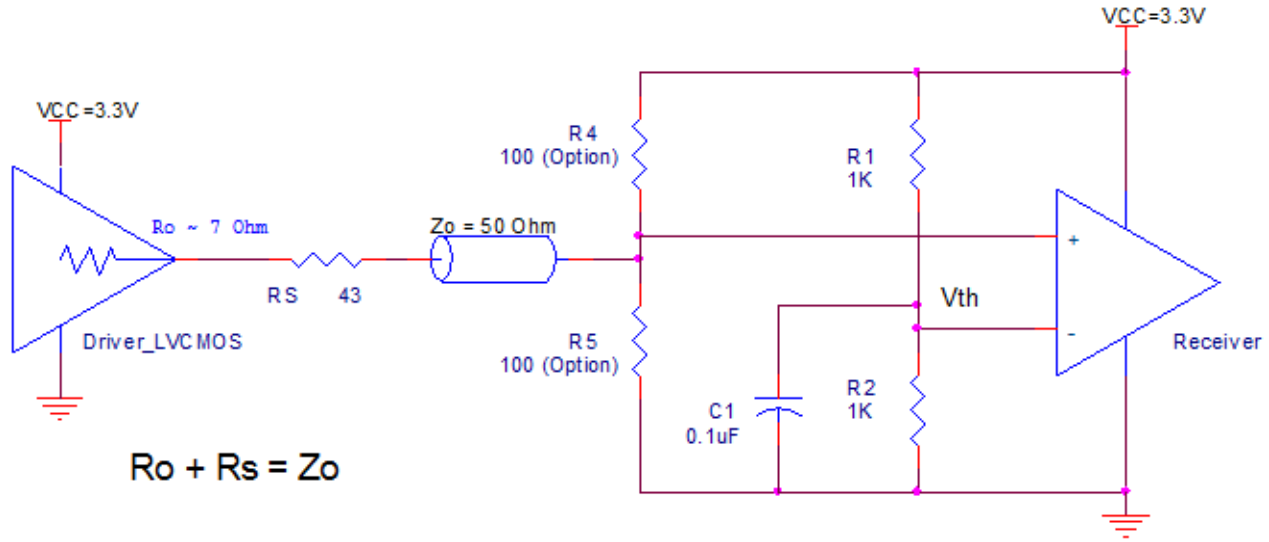


Figure 5. LVCMOS Overdrive XTAL Input

 


Increase R_s to reduce the amplitude

Figure 6. LVCMOS to 1.0V LVCMOS

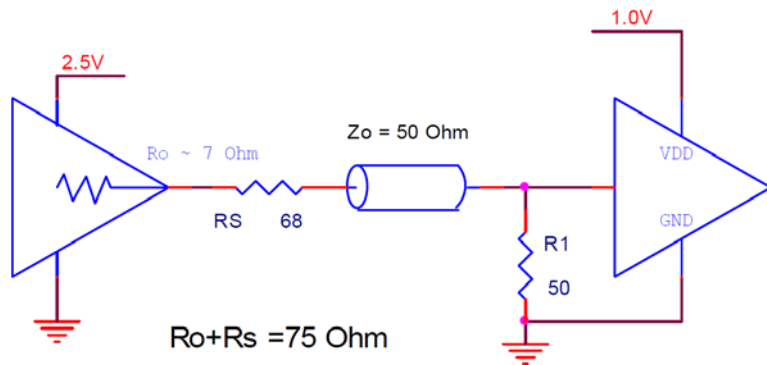

The R_s may need to be slightly adjusted to obtain proper logic high level at the receiver.

Figure 7. LVCMOS to 1.25V LVCMOS

 

The R_s may need to be slightly adjusted to obtain proper logic high level at the receiver.

Figure 8. LVCMOS to 3.3V LVCMOS, Series Termination

 


Figure 9. LVCMOS to 3.3V LVCMOS, Parallel Termination

 


Figure 10. LVCMOS to Differential Input with built-in Termination and DC Bias


 


Figure 11. Alternative LVCMOS to Differential Input with Built-in Termination and DC Bias

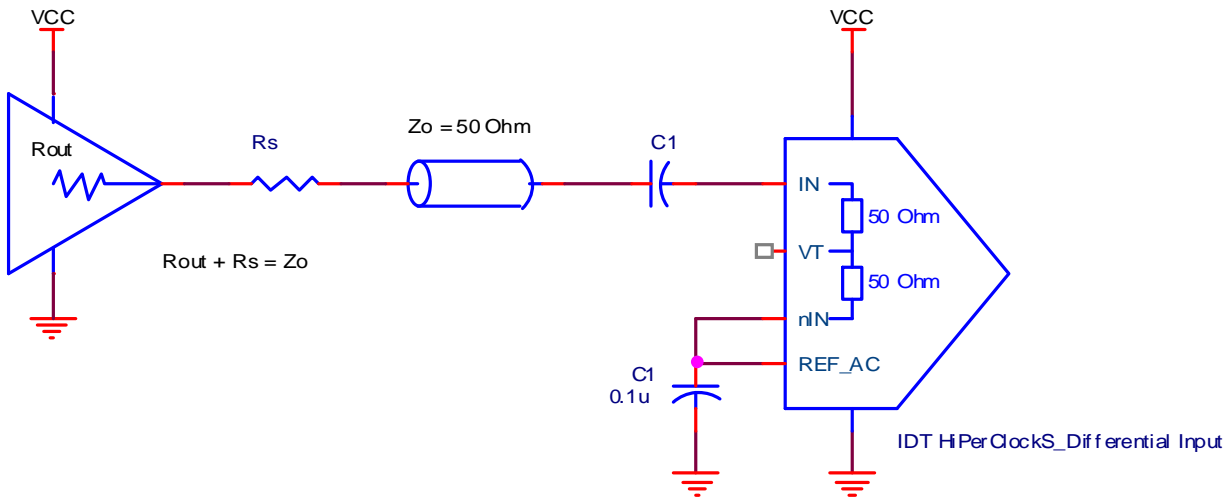

Increase R_s if amplitude reduction is necessary.

Figure 12. LVCMOS to 1V BCM56700


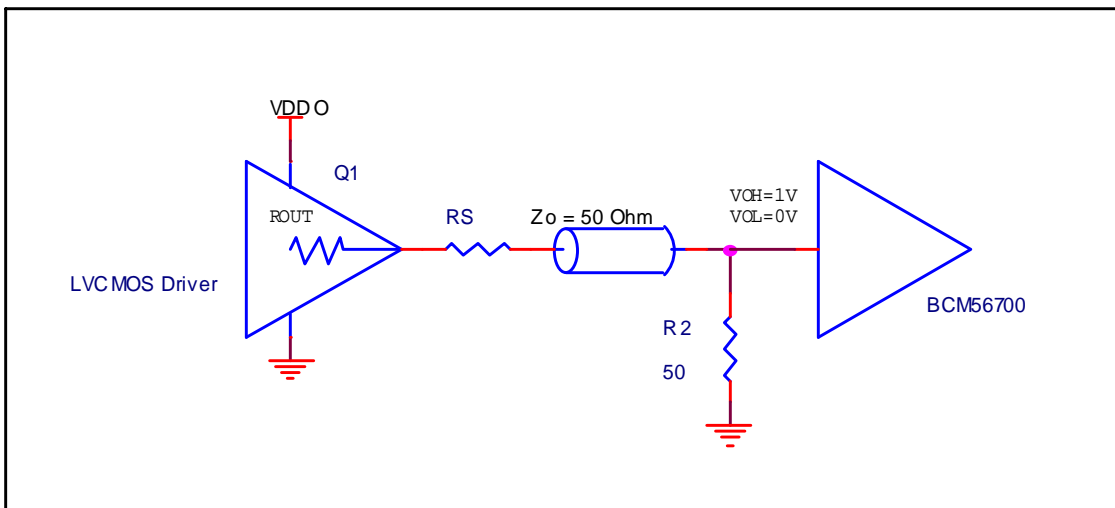


Figure 13. LVCMOS Tie N Outputs Together to Drive M Receivers

 

$$R_s = Z_o - (R_o \times M)/(N)$$

LVPECL Terminations

Figure 14. 3.3V LVPECL Standard Termination

 


Figure 15. 3.3V LVPECL Equivalent Termination

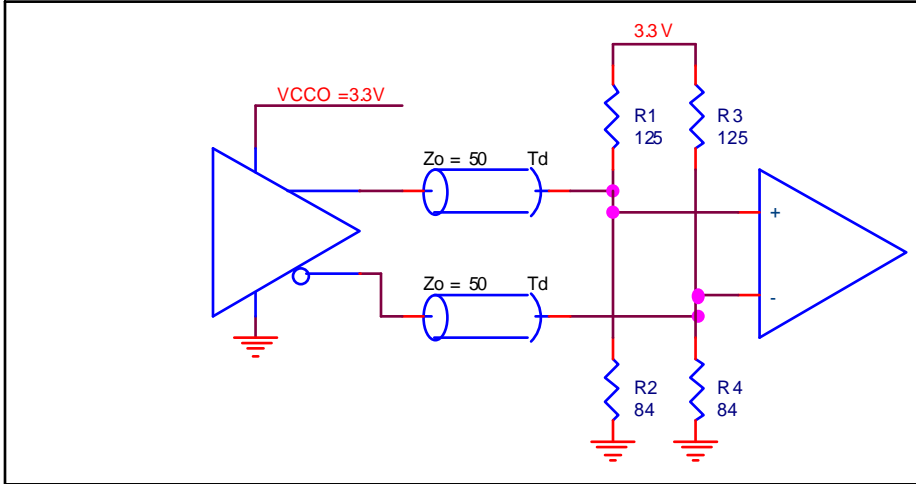


Figure 16. 3.3V LVPECL Equivalent Termination

 


Figure 17. 3.3V LVPECL Offset to VCC - 2V

 


Figure 18. 3.3V LVPECL Offset to VCC - 1.3V

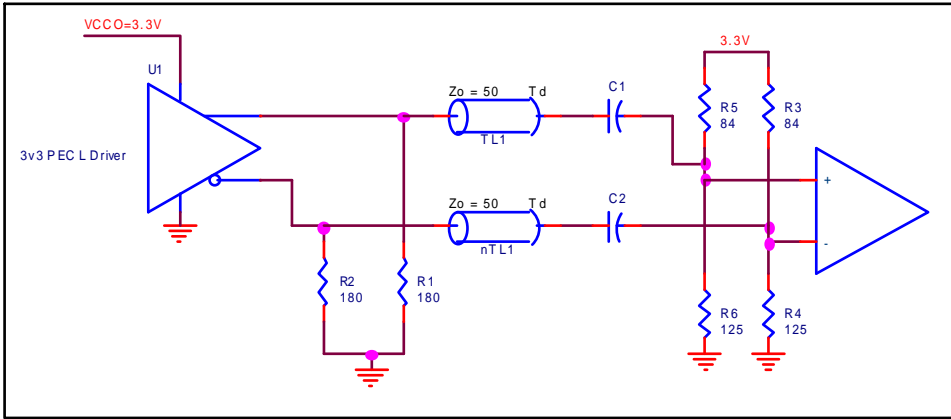


Figure 19. 3.3V LVPECL Driver to 1.5V SSTL

 


Figure 20. 3.3V LVPECL Driver to 1.8V SSTL

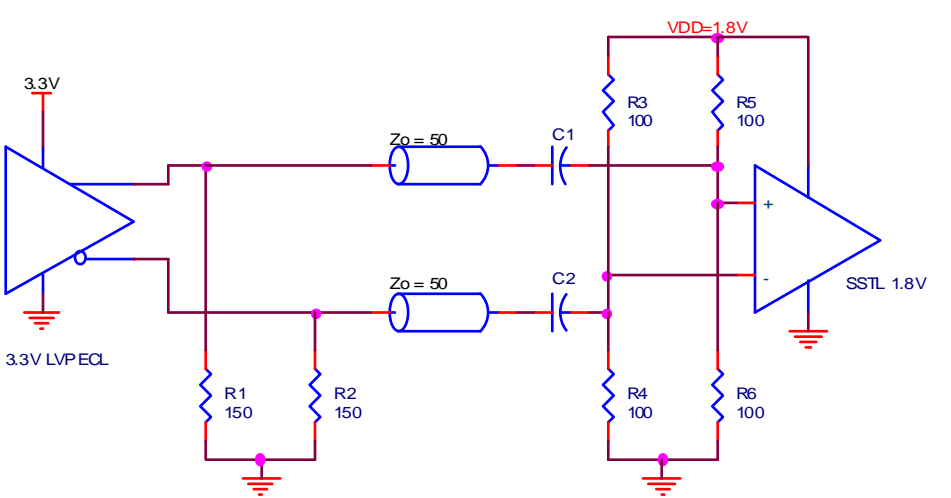


Figure 21. 3.3V LVPECL Driver to 1.8V SSTL, Thevenin Termination


 


Figure 22. 3.3V LVPECL Termination Amplitude Reduction

 

Larger R3/R4 resistance further reduces the amplitude.

Figure 23. 3.3V LVPECL to 2.5 Differential Input with High DC Offset Requirement

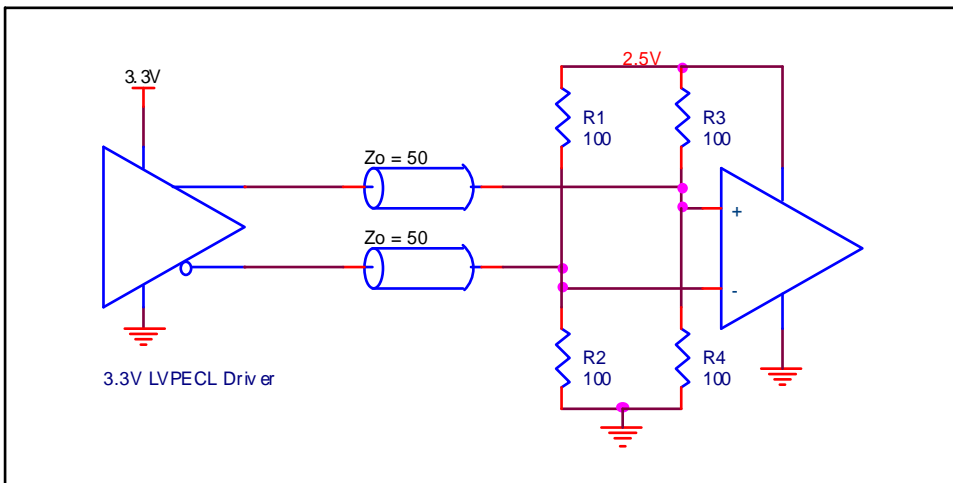


Figure 24. 3.3V LVPECL to LVDS, Option 1

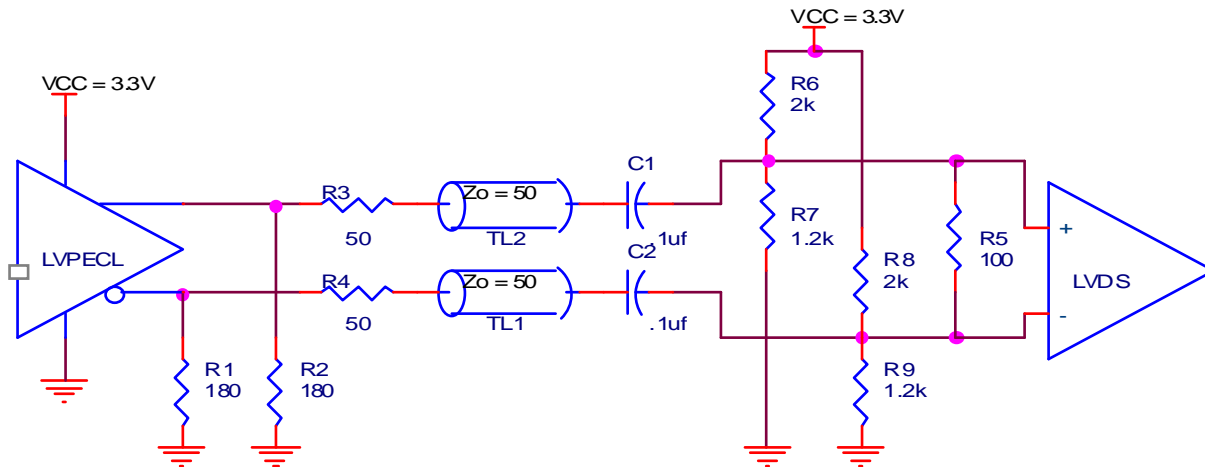


Figure 25. 3.3V LVPECL to LVDS, Option 2


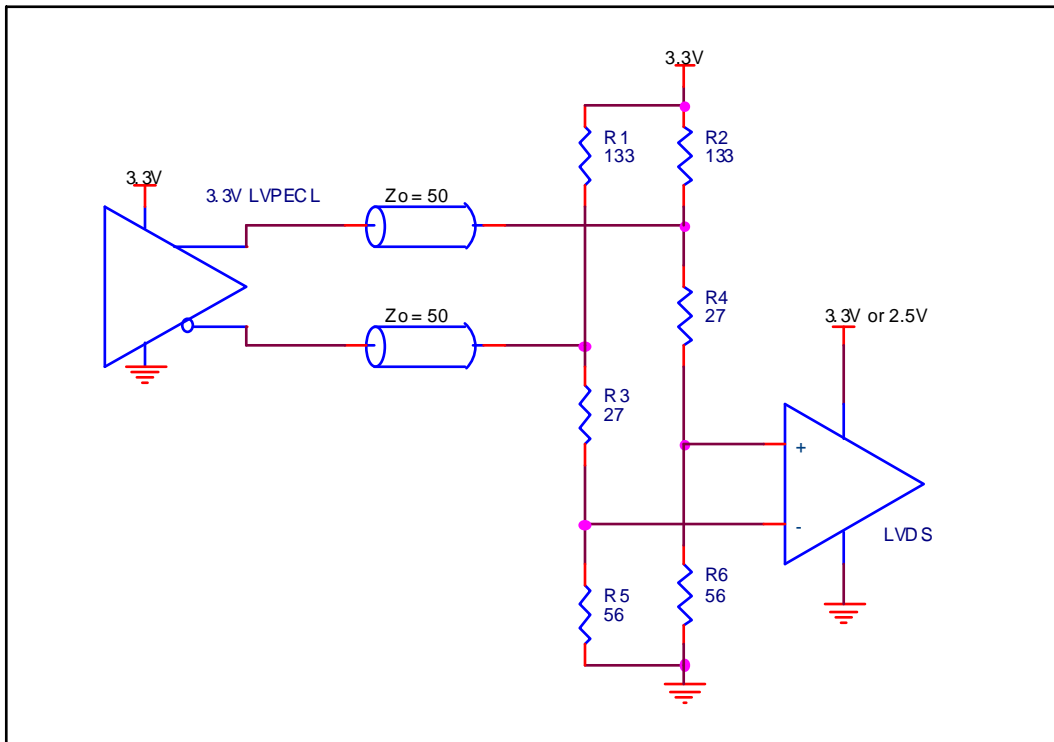


Figure 26. LVPECL to HSTL, Receiver VCC=1.5V and V_REF=0.75V, Option 1

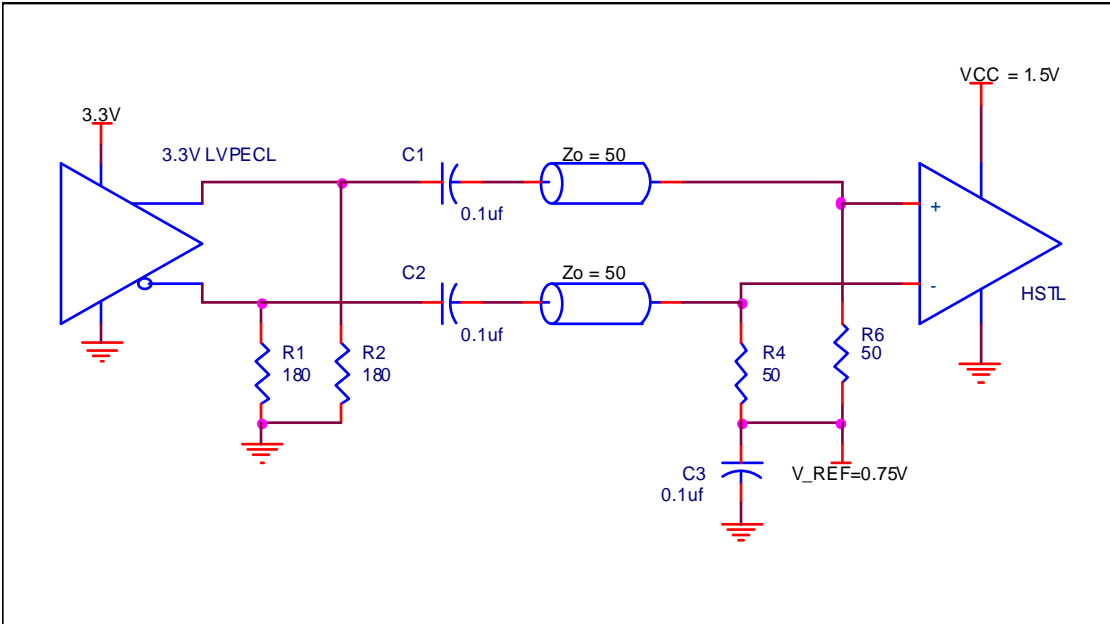

Use this option if there is 0.75V rail available.

Figure 27. LVPECL to HSTL, Receiver VCC=1.5V and V_REF=0.75V, Option 2

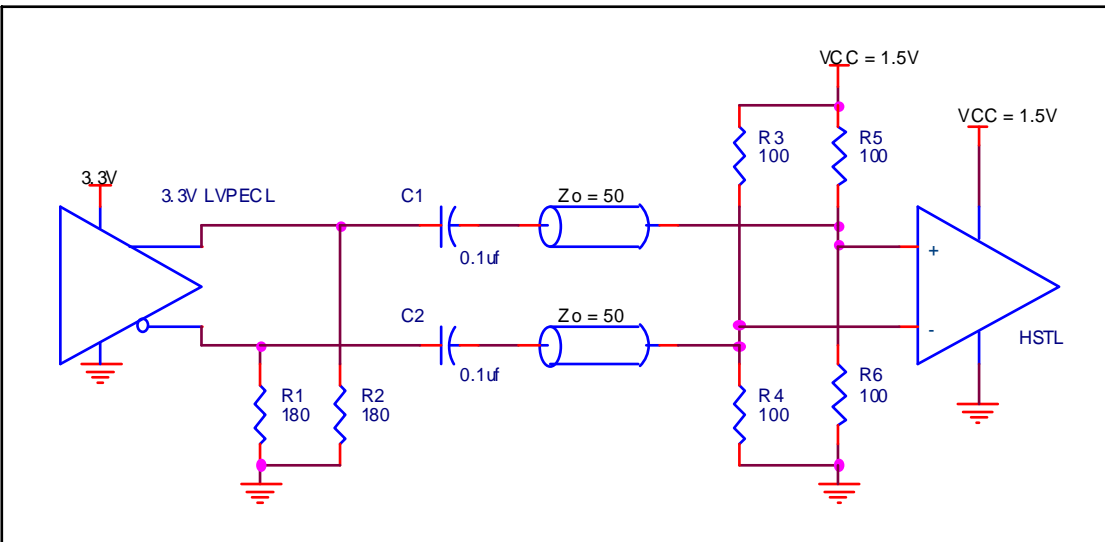


Figure 28. LVPECL to HSTL, Receiver VCC=3.3V

 


Figure 29. LVPECL to HCSL (DCM)

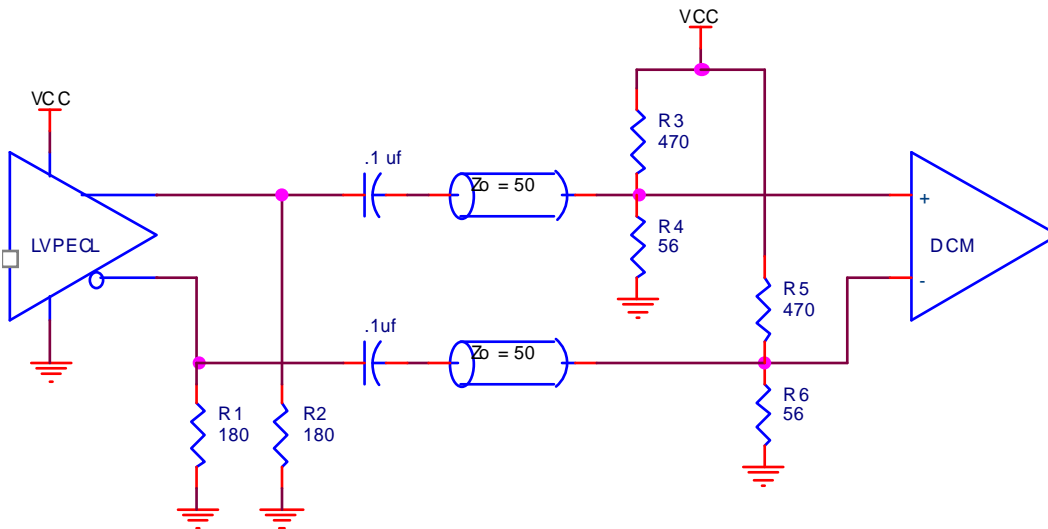


Figure 30. 3.3V LVPECL to Broadcom BCM5785

 


Figure 31. LVPECL to Differential 100ohm DC, 10K Bias

 


Figure 32. LVPECL to 2.5 LVCMOS

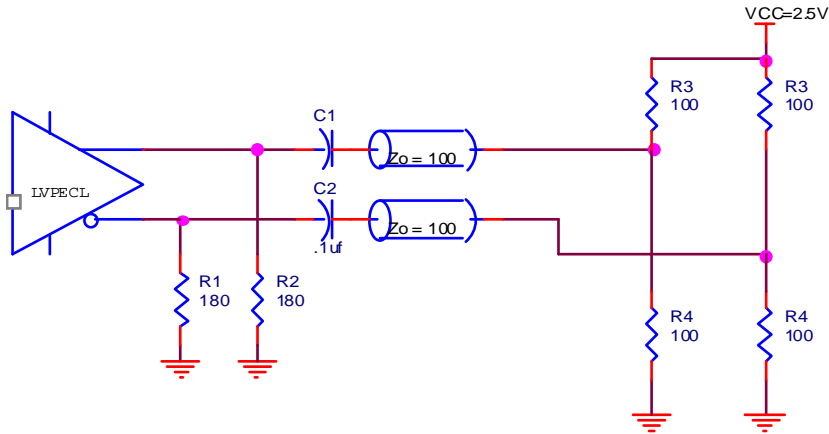


Figure 33. 3.3V LVPECL to 2.5V Different Input with LVDS DC Offset Level Requirement

 


Figure 34. 3.3V LVPECL to PCML, Option 1

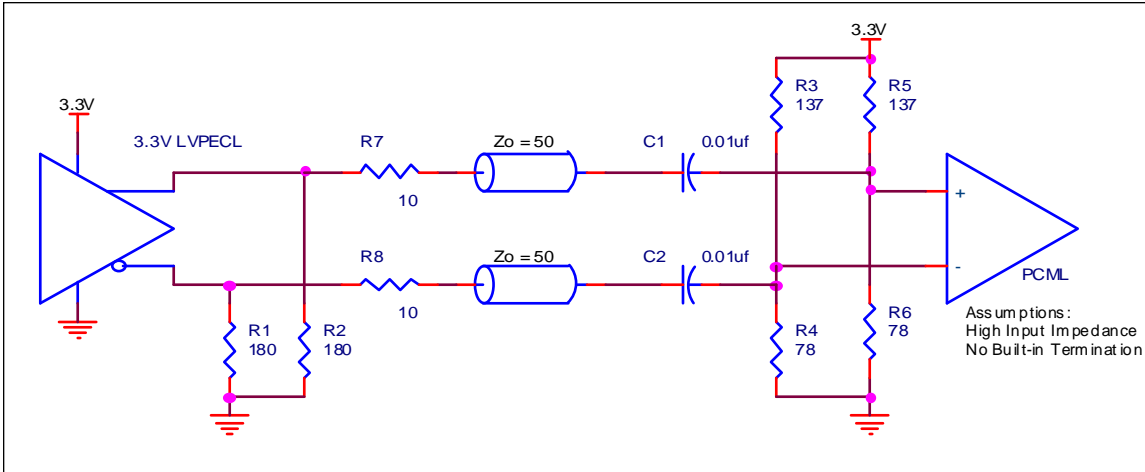


Figure 35. 3.3V LVPECL to PCML, Option 2

 


Figure 36. 3.3V LVPECL Driving Receiver with Built-in Termination and Built-in Self Bias

 


Figure 37. 3.3V LVPECL to HCSL

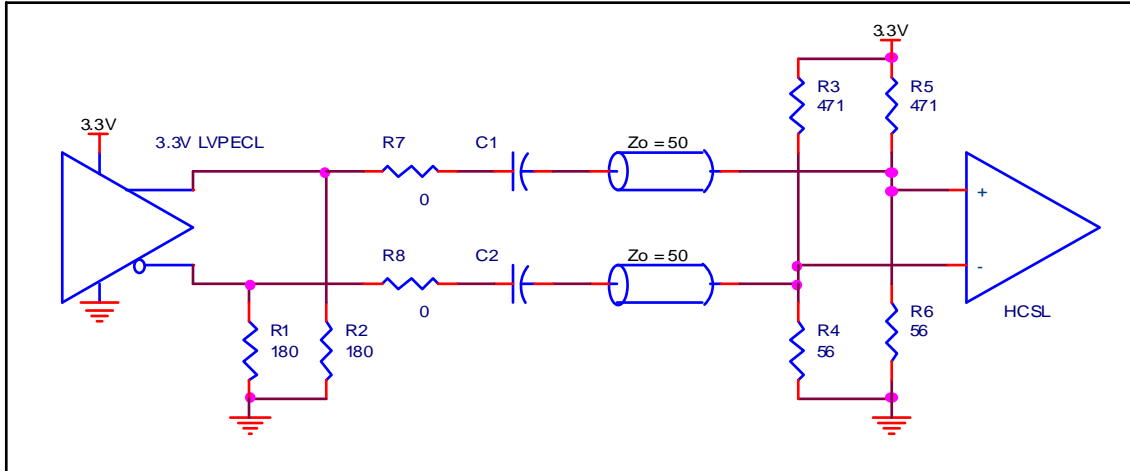


Figure 38. 3.3V LVPECL to 1.8V LVCMOS Interface

 


Figure 39. 3.3V LVPECL to 1.8V Differential Interface, Option 1

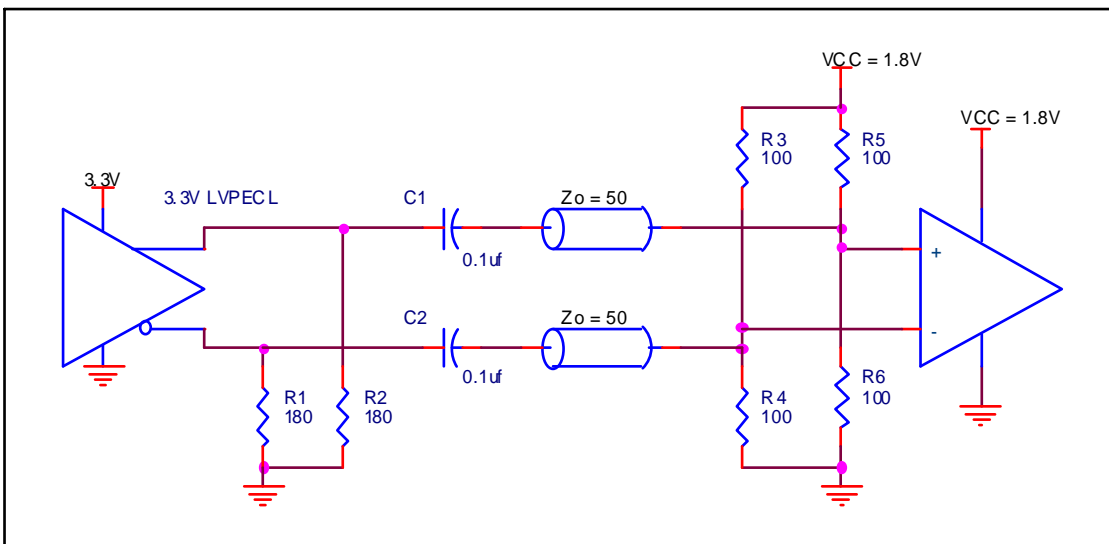


Figure 40. 3.3V LVPECL to 1.8V Differential Interface, Option 2

 


Figure 41. 3.3V LVPECL to 0.65V DC Offset

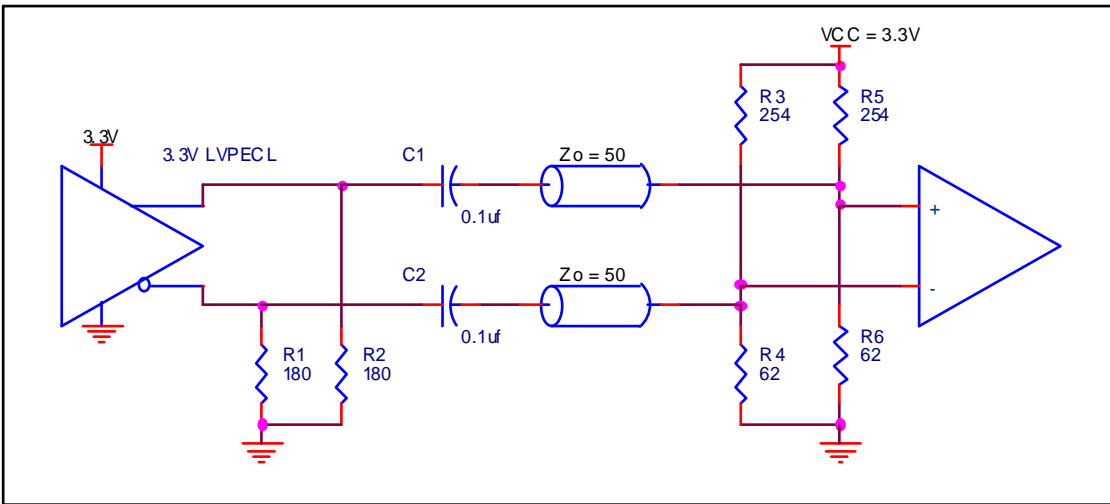


Figure 42. 3.3V LVPECL to CML

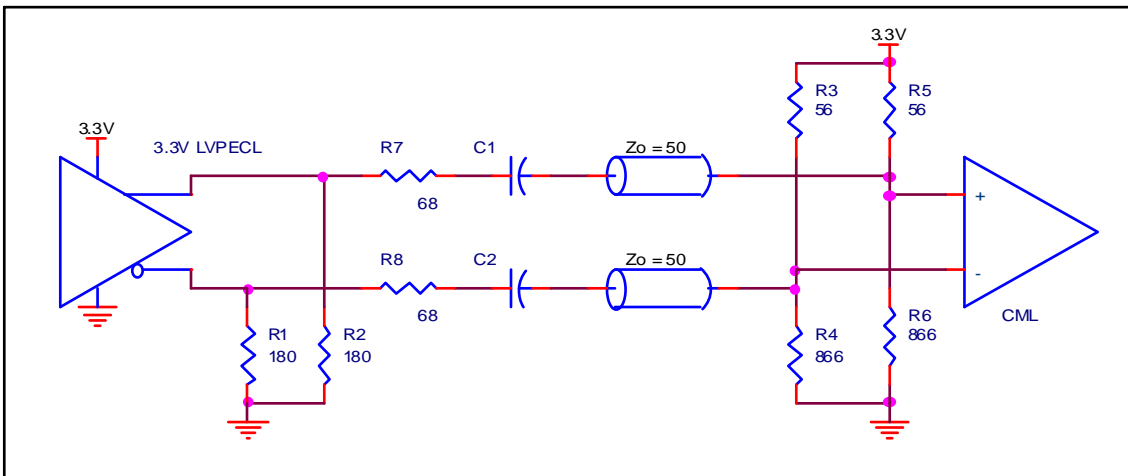


Figure 43. 3.3V LVPECL to 2.5V SSTL 2 Interface with VDD/2 Voltage Source

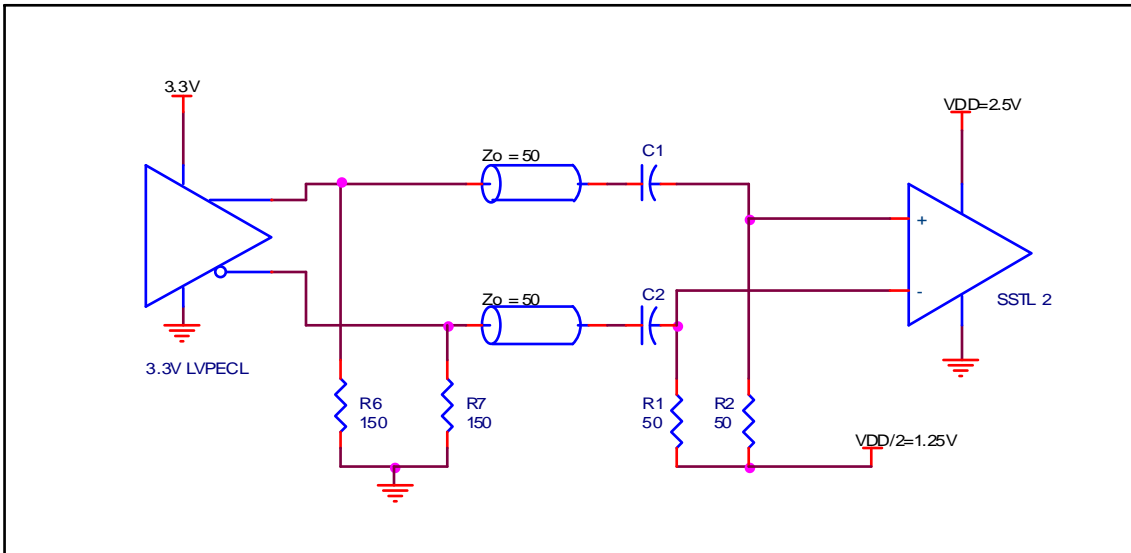


Figure 44. 3.3V LVPECL to 2.5V SSTL 2 Interface without VDD/2 Voltage Source

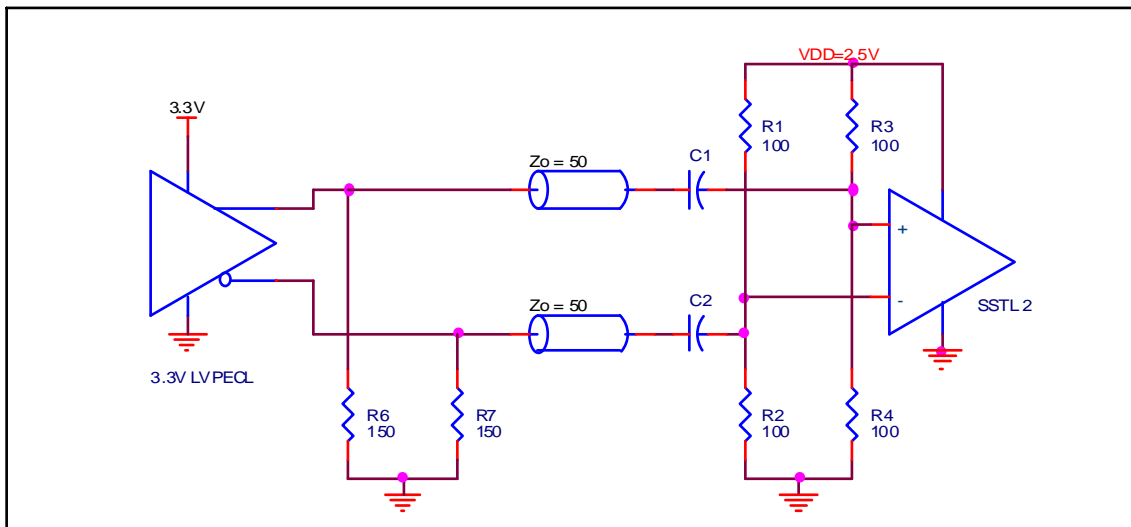


Figure 45. 2.5V LVPECL Standard Termination

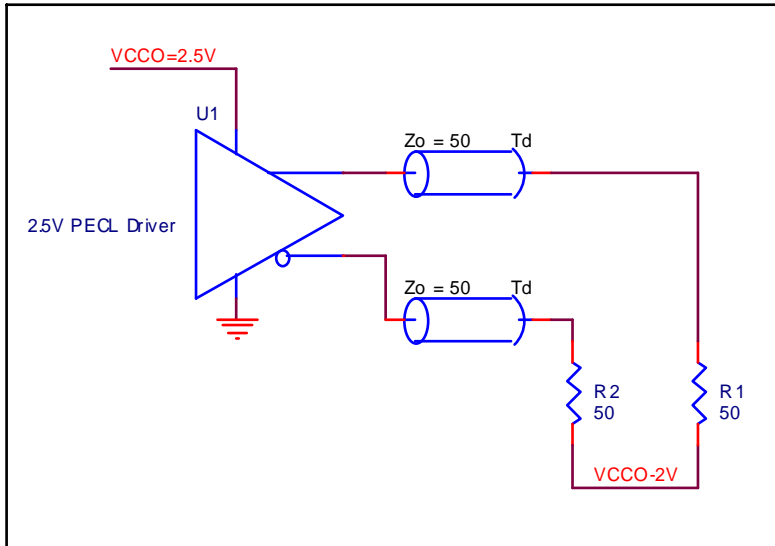


Figure 46. 2.5V LVPECL Equivalent Termination

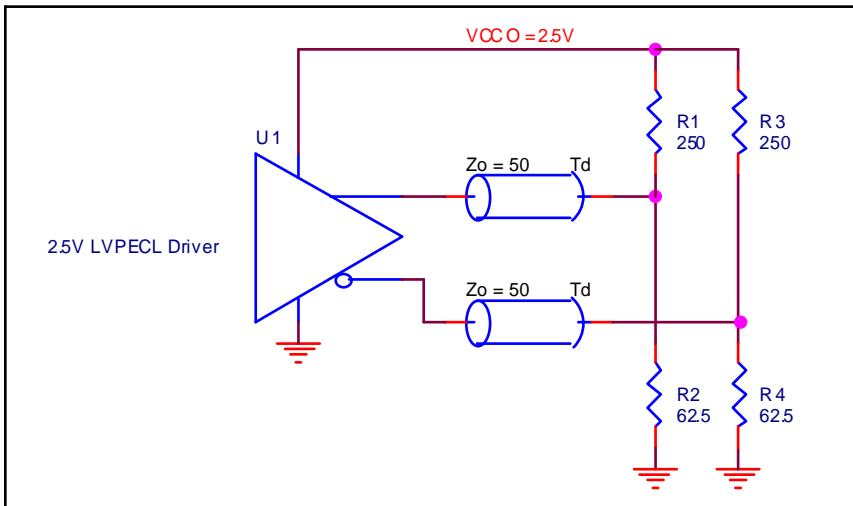


Figure 47. 2.5V LVPECL Equivalent Termination

 


Figure 48. 2.5V LVPECL Termination, No Receiver

 


Figure 49. 2.5V LVPECL to Differential Input (CLK/nCLK) Interface, Option 1

 


Figure 50. 2.5V LVPECL to Differential Input (CLK/nCLK) Interface, Option 2

 


Figure 51. 2.5V LVPECL to Differential Input (CLK/nCLK) Interface, Option 3

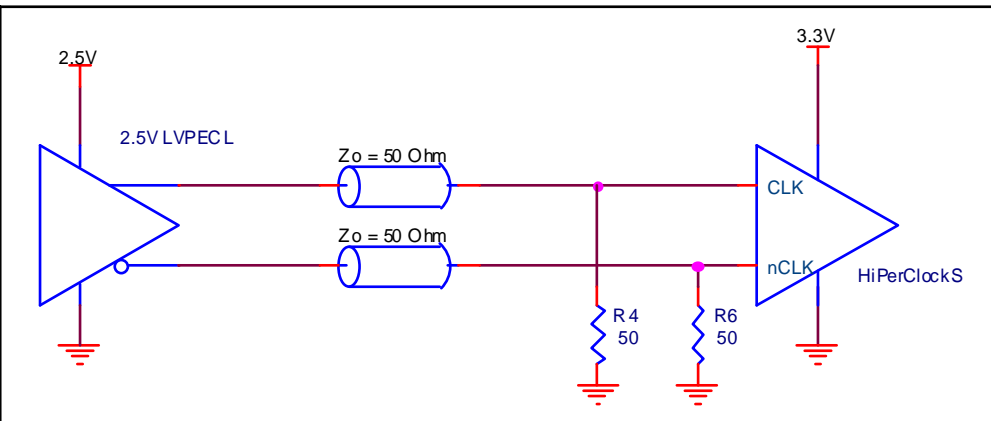


Figure 52. 2.5V LVPECL to 0.8V DC offset Receiver

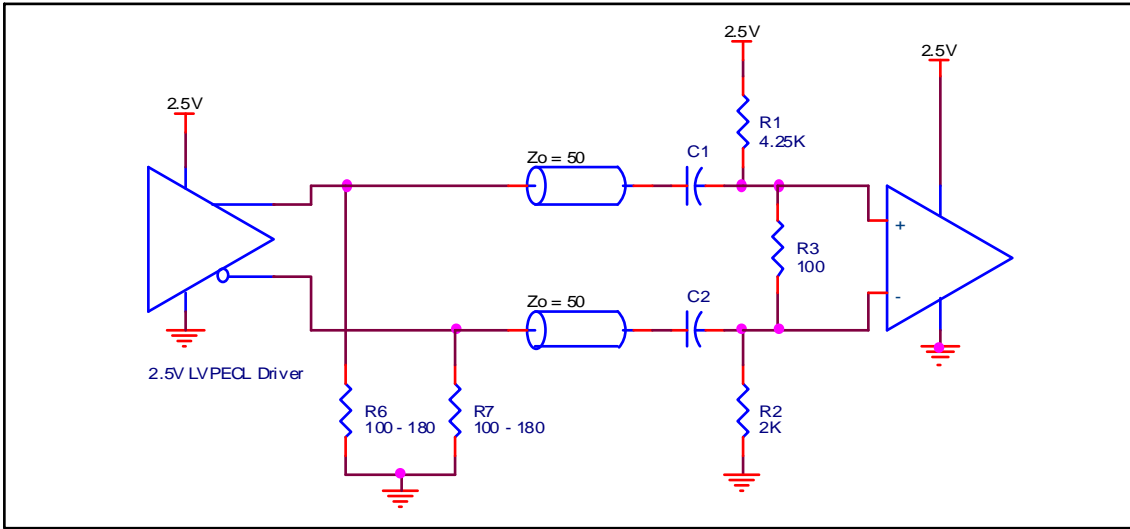


Figure 53. LVPECL, AC-Coupled to Receiver with no DC Offset Requirement
40

 


Figure 54. LVPECL to XTAL

 


Figure 55. LVPECL Short Trace Termination

 


Figure 56. LVPECL to Single-Ended LVPECL, Option 1

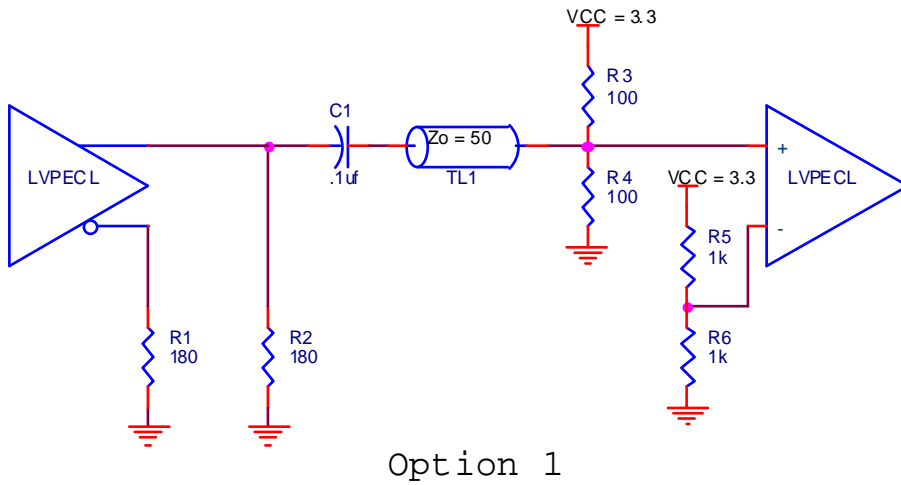


Figure 57. LVPECL to Single-Ended LVPECL, Option 2


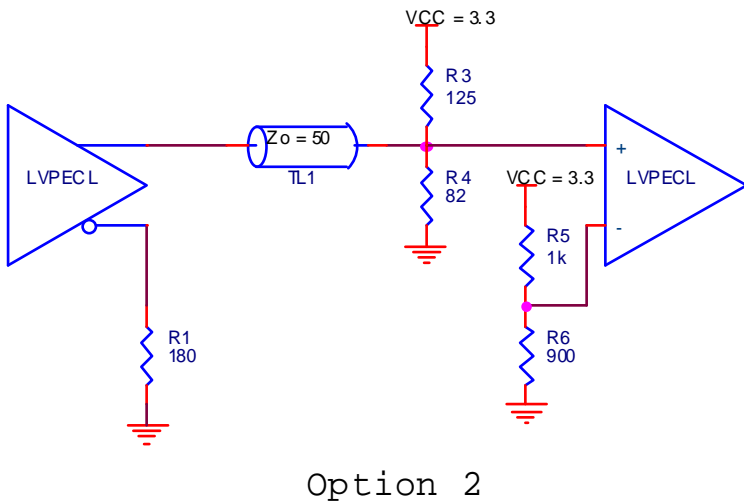


Figure 58. LVPECL to Single-Ended LVPECL with VBB Bias, Option 1

 

Re-biasing positive side of input to $V_{cc} - 1.3V$ to match VBB

Figure 59. LVPECL to Single-Ended LVPECL with VBB Bias, Option 2

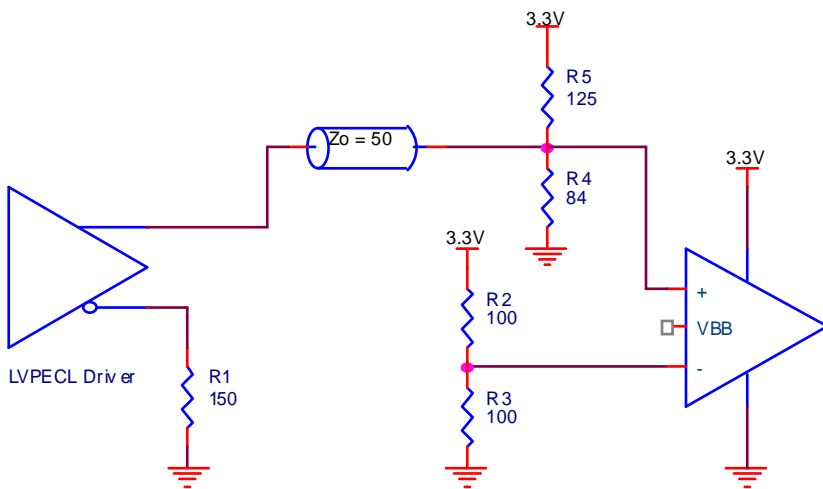


Figure 60. LVPECL to Single-Ended LVPECL with VBB Bias, Option 3


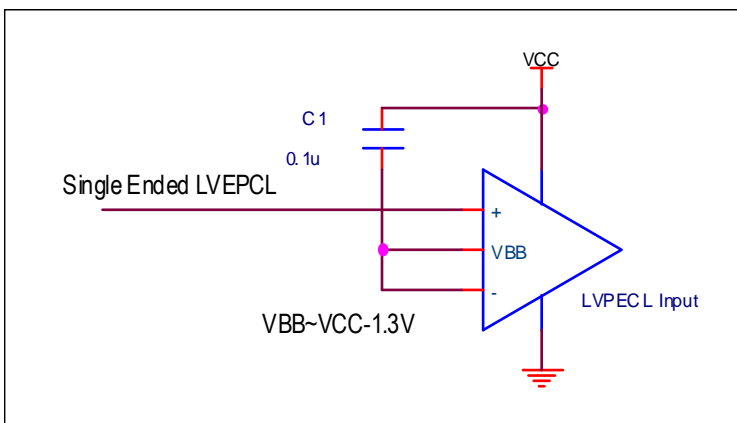


Figure 61. LVPECL to Single-Ended LVPECL with VBB Bias, Option 4

 

Re-biasing both sides of the input using VBB.

Figure 62. LVPECL to HCSL (DCM)

 


Figure 63. LVPECL Drives Two Receivers

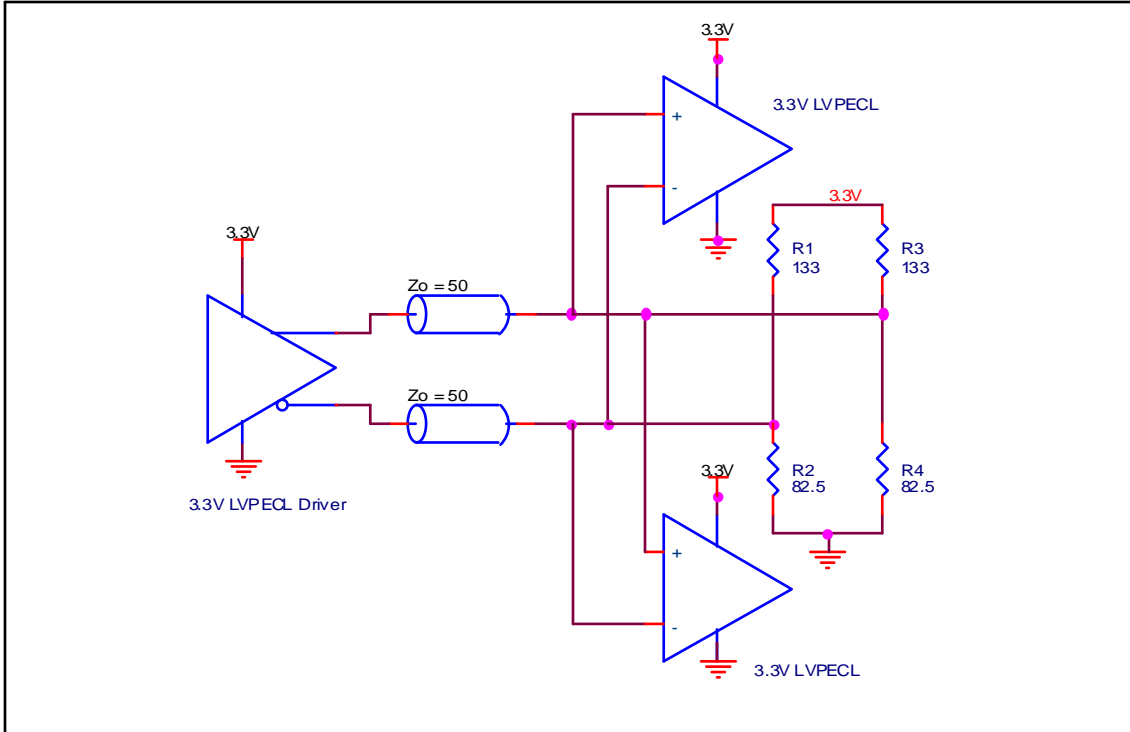


Figure 64. 3.3V LVPECL to AMD8132

 


Figure 65. 2.5V LVPECL to AMD8132

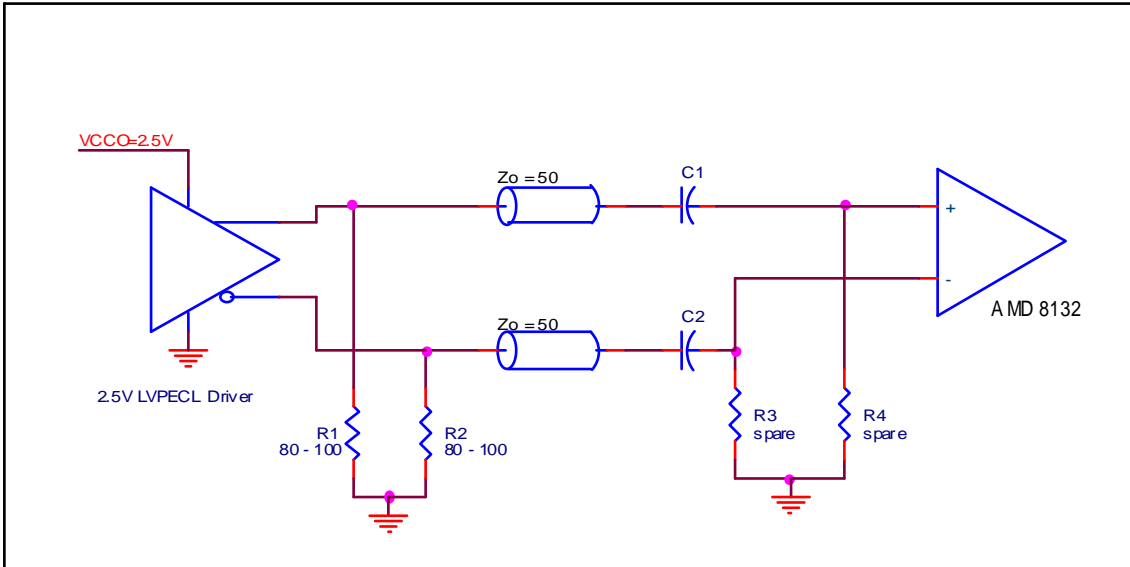


Figure 66. 3.3V LVPECL to AMD K8 CPU CLK Input


 


Figure 67. 2.5V LVPECL to AMD K8 CPU CLK Input

 

LVDS Terminations

Figure 68. LVDS Termination

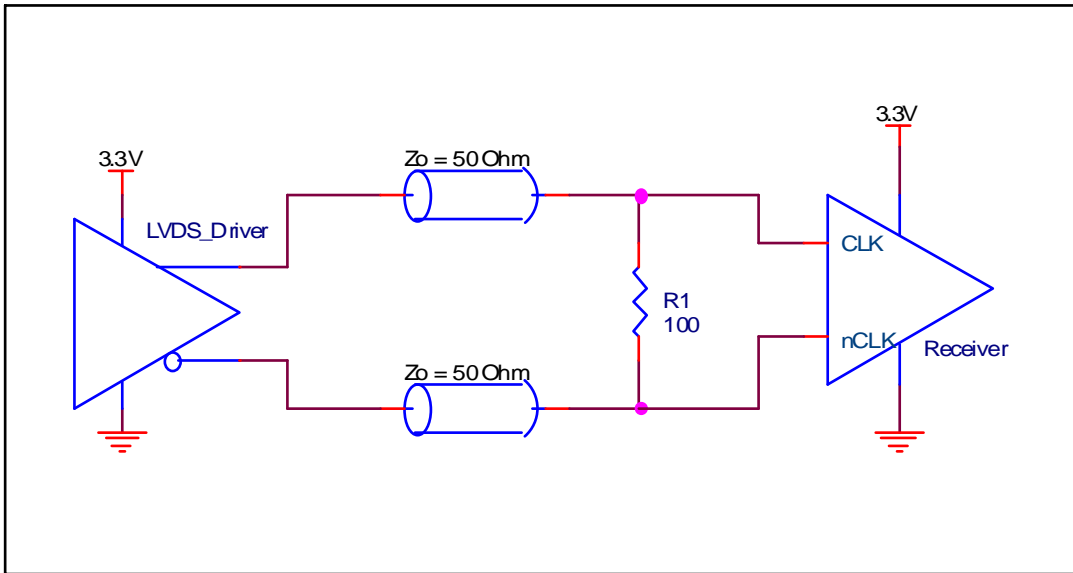


Figure 69. LVDS AC-Coupling, Option 1

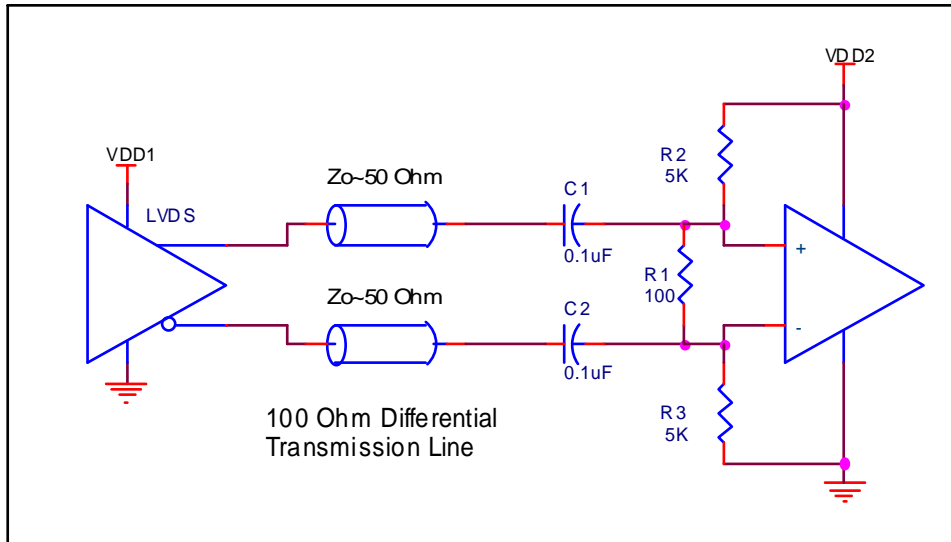


Figure 70. LVDS AC-Coupling, Option 2

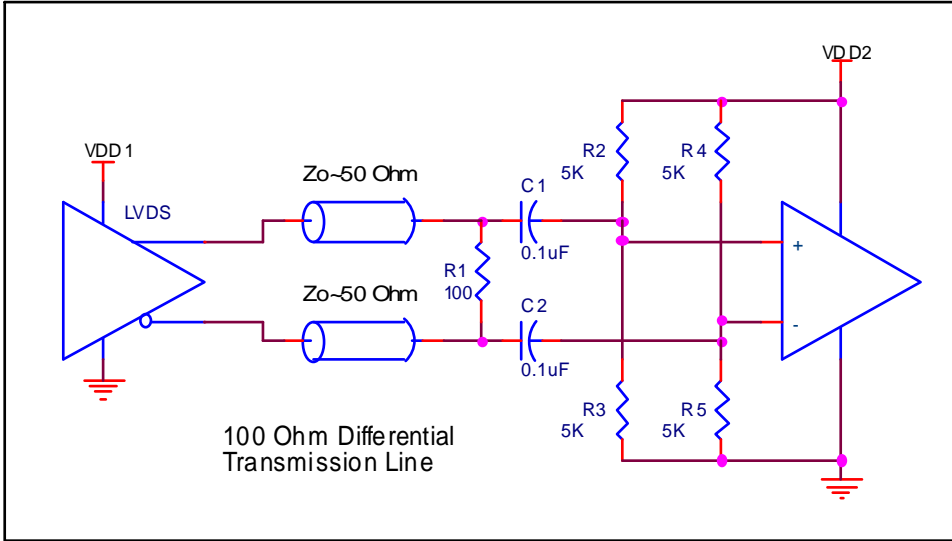


Figure 71. 3.3V LVDS to 2.5 LVDS

 


Figure 72. LVDS to CML

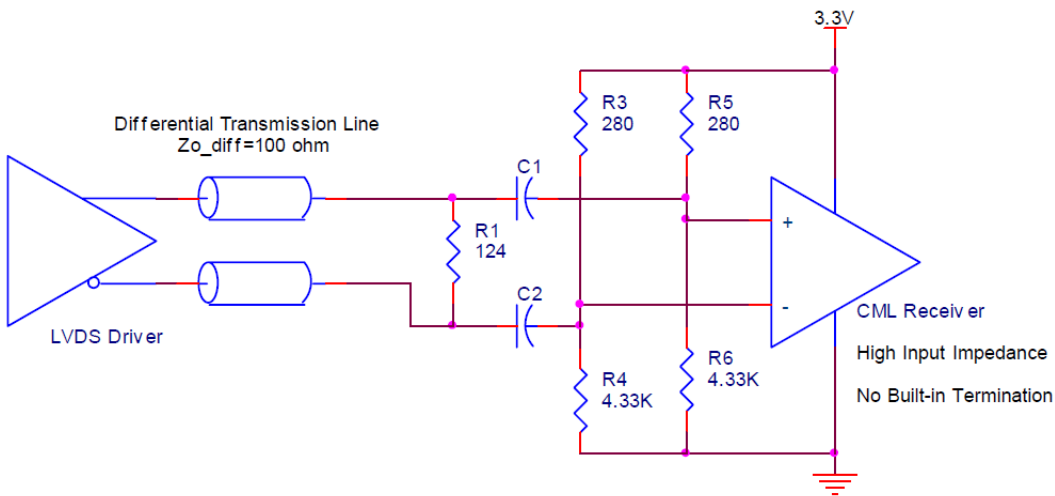


Figure 73. LVDS AC-Coupled to Built-In Termination



 


Figure 74. LVDS (Voltage Source) Amplitude Reduction

 

Increasing R2/R3 reduces the amplitude.

Figure 75. LVDS (Current Source) Amplitude Reduction

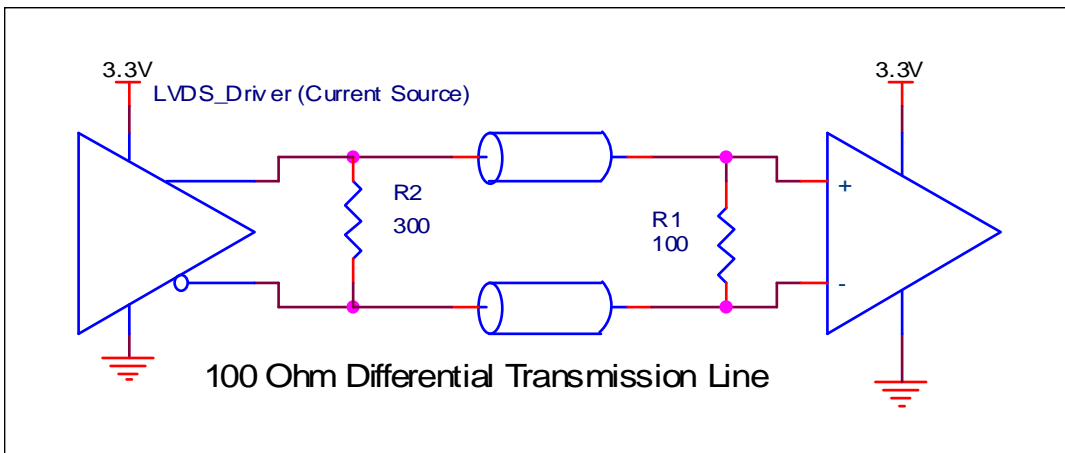

Increasing R2 reduces the amplitude.

Figure 76. LVDS (Current Source) to 1.5V VOS

 


Figure 77. LVDS to 0.6V DC Offset, Option 1

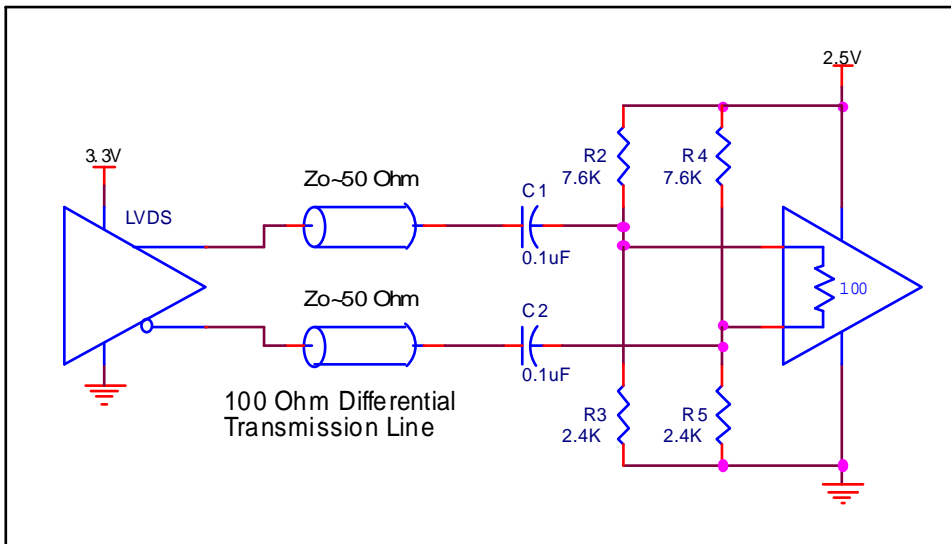


Figure 78. LVDS to 0.6V DC Offset, Option 2

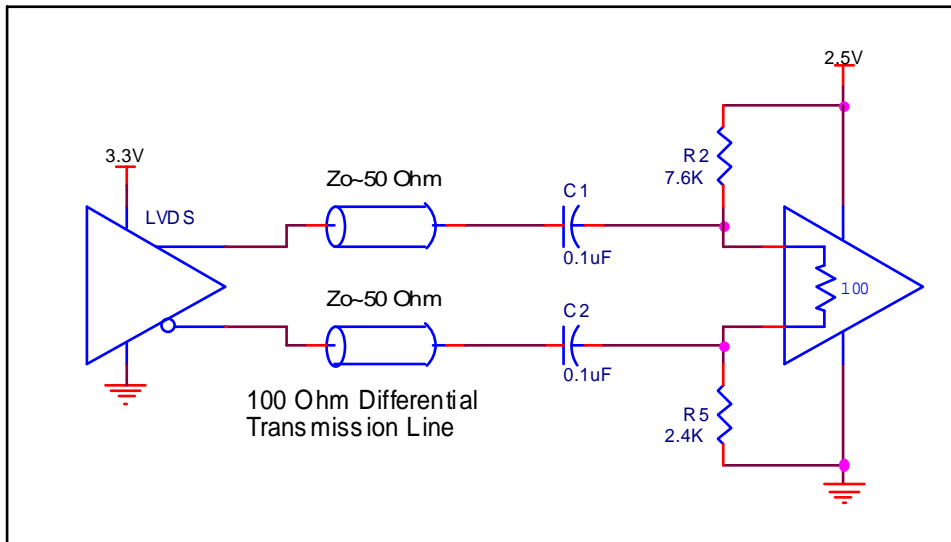


Figure 79. LVDS to XTAL

 


Figure 80. LVDS to IDT PES24T6G2 HCSL Input Interface

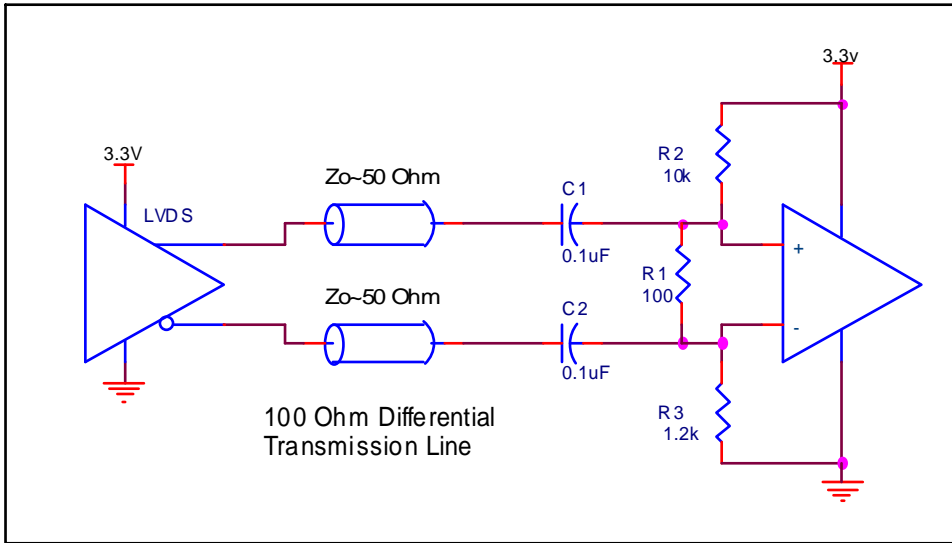


Figure 81. LVDS to PCML

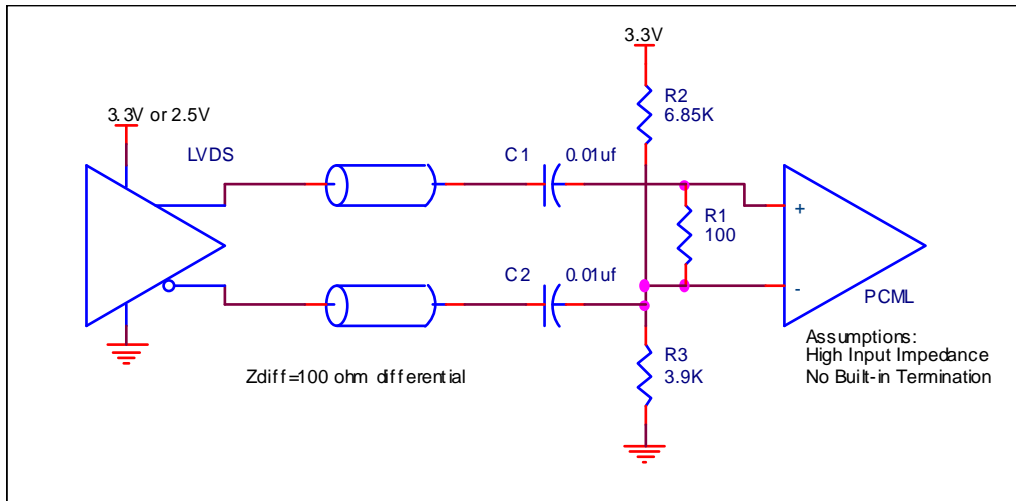


Figure 82. LVDS Differential Duty Cycle Improvement


 


Figure 83. LVDS to 50-ohm Scope, Non-Floating Supply

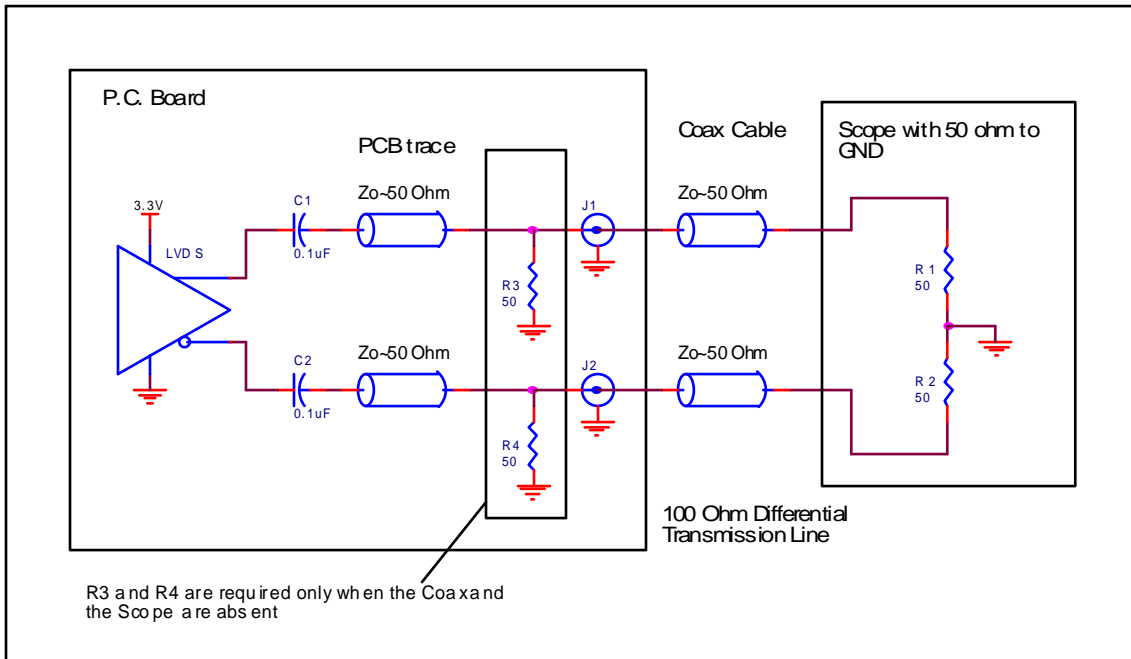

HSTL Terminations

Figure 84. HSTL Standard Termination

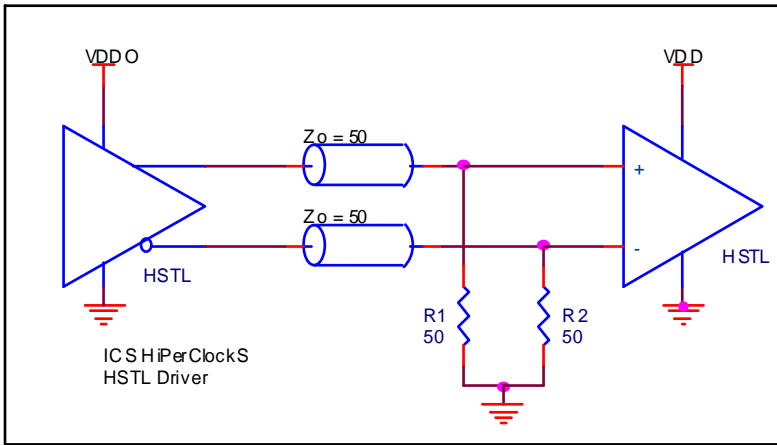


Figure 85. HSTL to 3.3V LVPECL

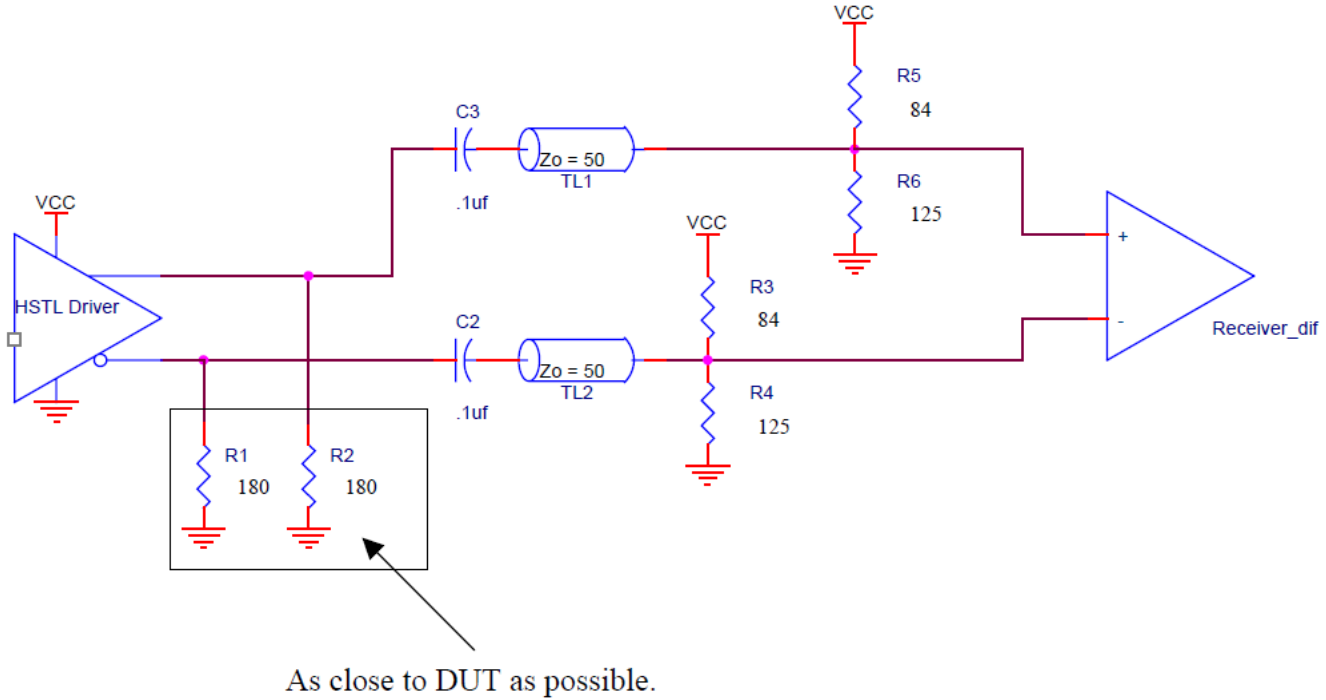


Figure 86. HSTL to Xilinx Spartan 1.8V HSTL II , Option 1

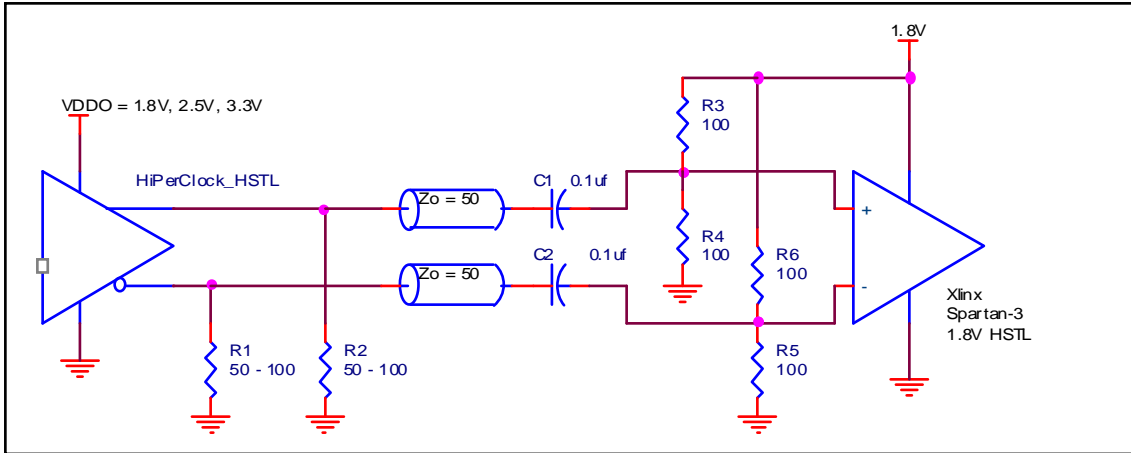


Figure 87. HSTL to Xilinx Spartan 1.8V HSTL II, Option 2

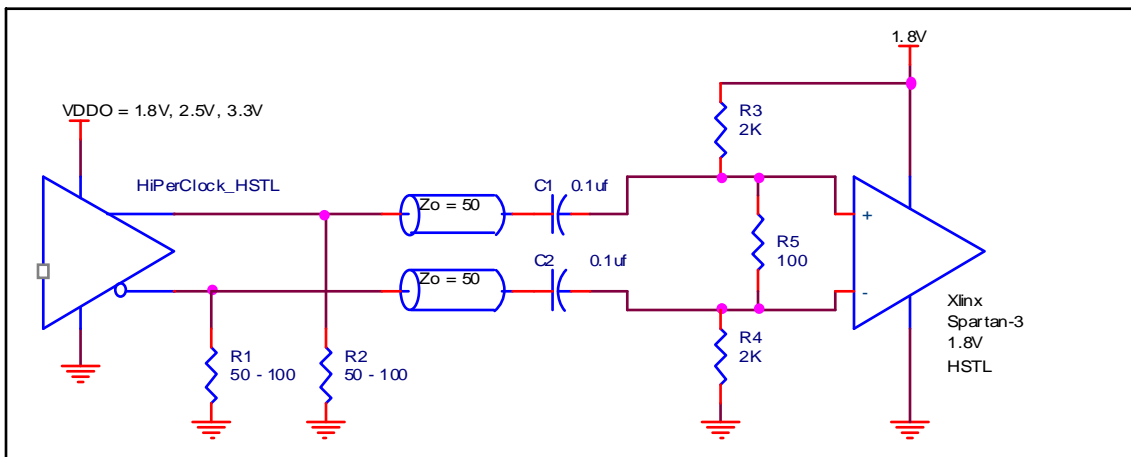


Figure 88. HSTL to LVDS



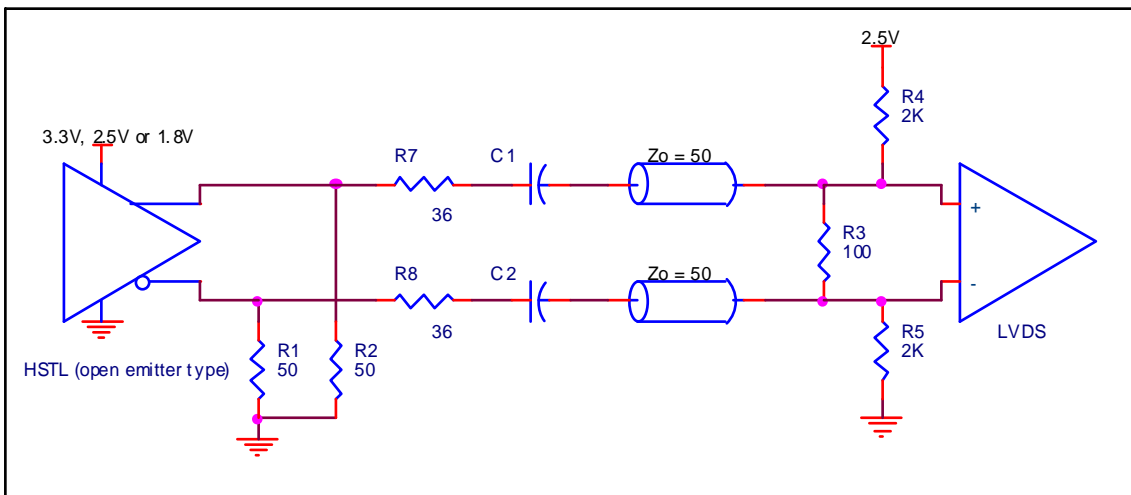


Figure 89. HSTL to 1.8V SSTL, Option 1

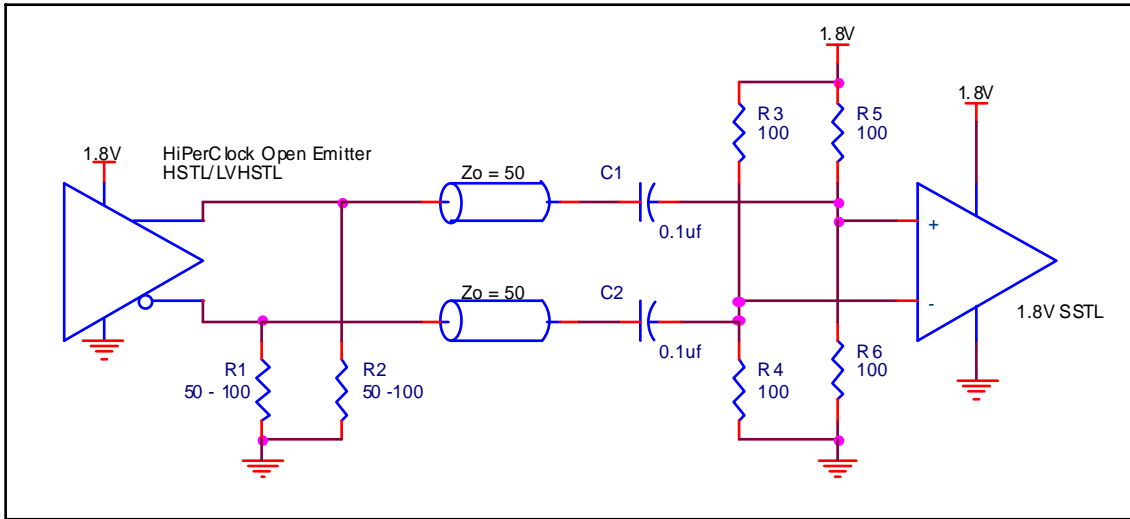

Termination for 50-ohm transmission line

Figure 90. HSTL to 1.8V SSTL, Option 2

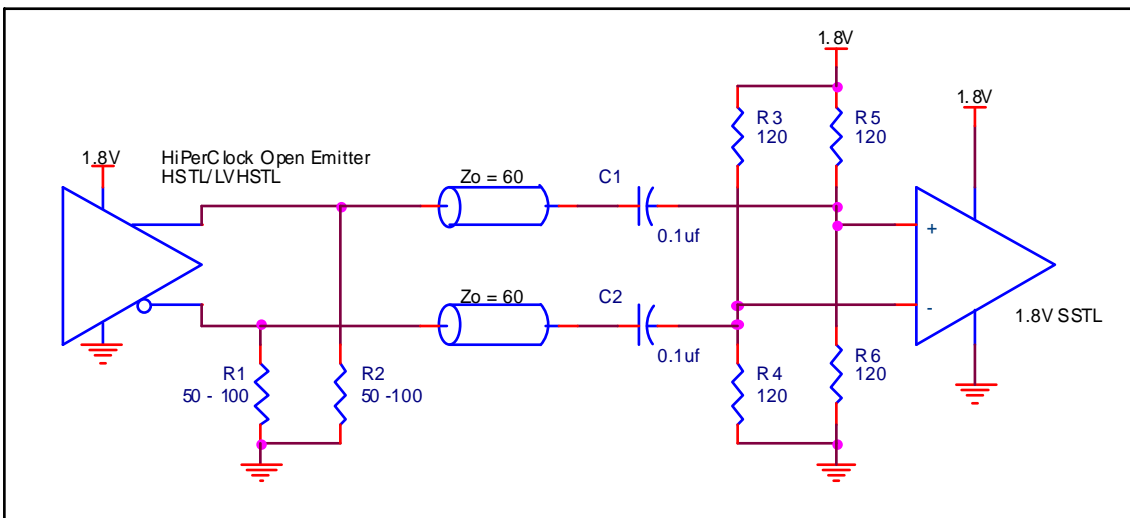

Termination for 60 ohm transmission line

Figure 91. HSTL to 1.5V HSTL, DC-Couple

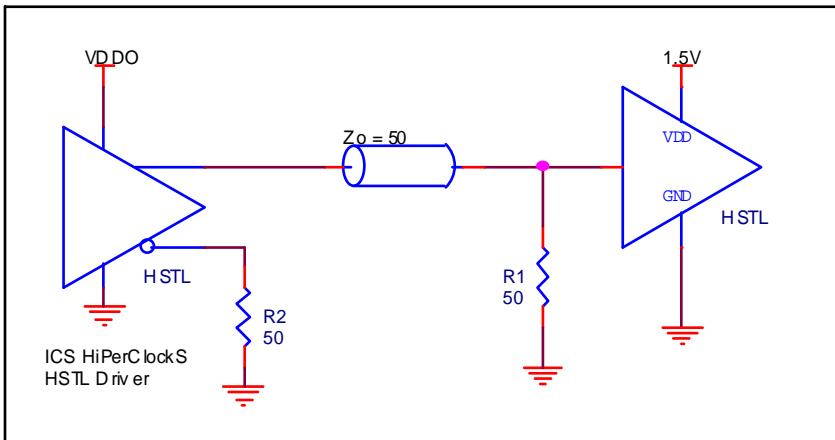


Figure 92. HSTL to 1.5V HSTL, AC-Couple

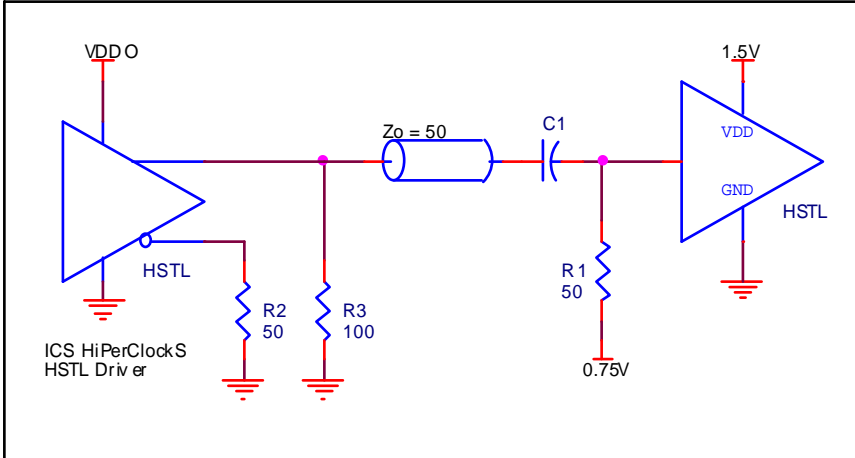


Figure 93. 1.5V HSTL Push-Pull Driver to Differential Input with 0.75V Bias

 


Figure 94. 1.5V HSTL Push-Pull Driver Differential Input Voltage Divider Bias


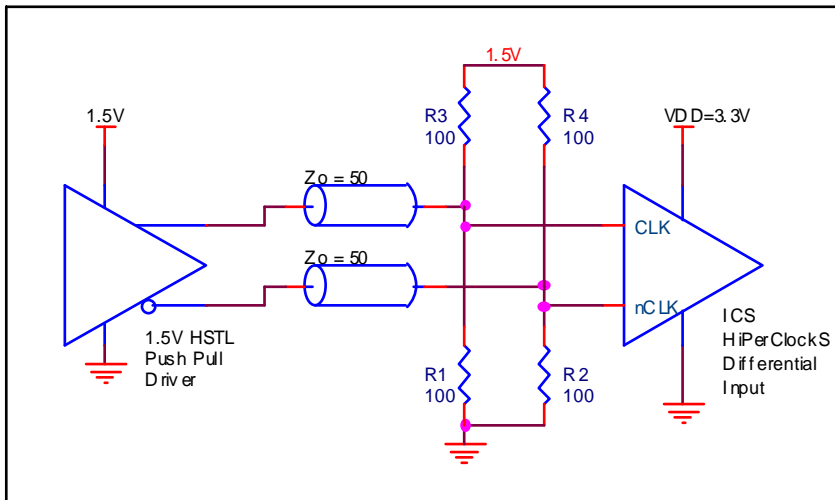


Figure 95. HSTL to DDR2

 

HCSL Terminations

Figure 96. HCSL to Differential Input Interface with Pulldown at the Driver

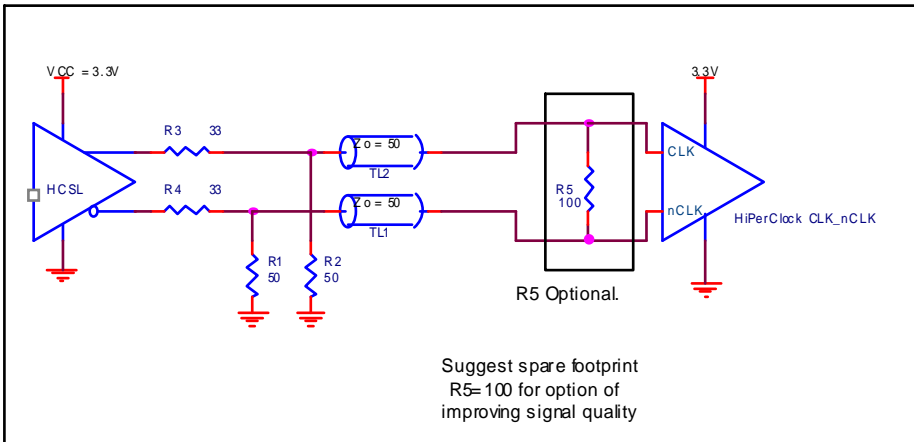


Figure 97. HCSL to Differential Input Interface with Pulldown at the Receiver

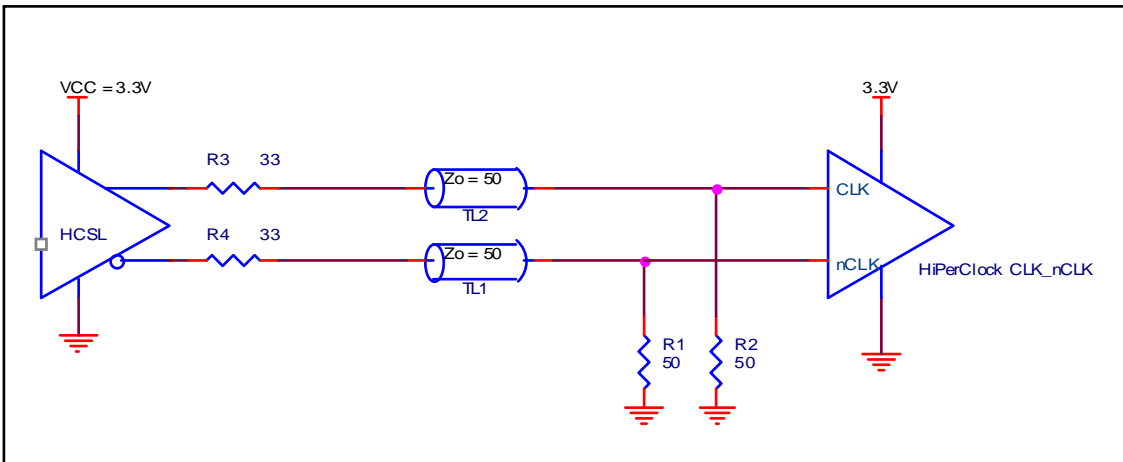


Figure 98. HCSL to LVPECL

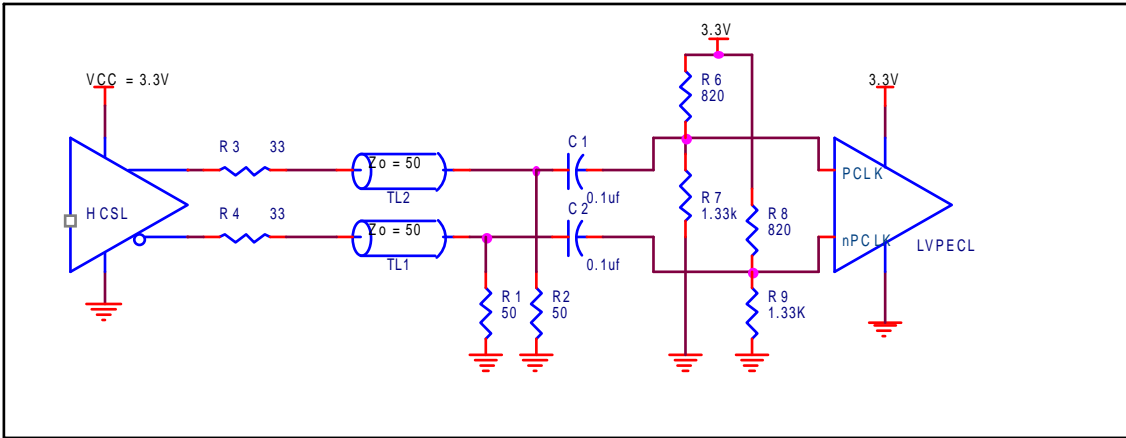


Figure 99. HCSL to IDT Differential PCLK/nPCLK, Option 1

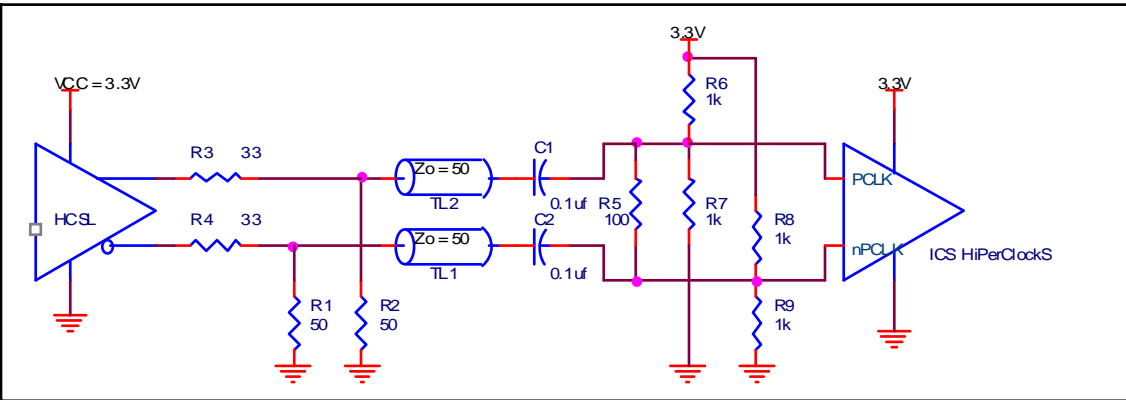


Figure 100. HCSL to IDT Differential PCLK/nPCLK, Option 2

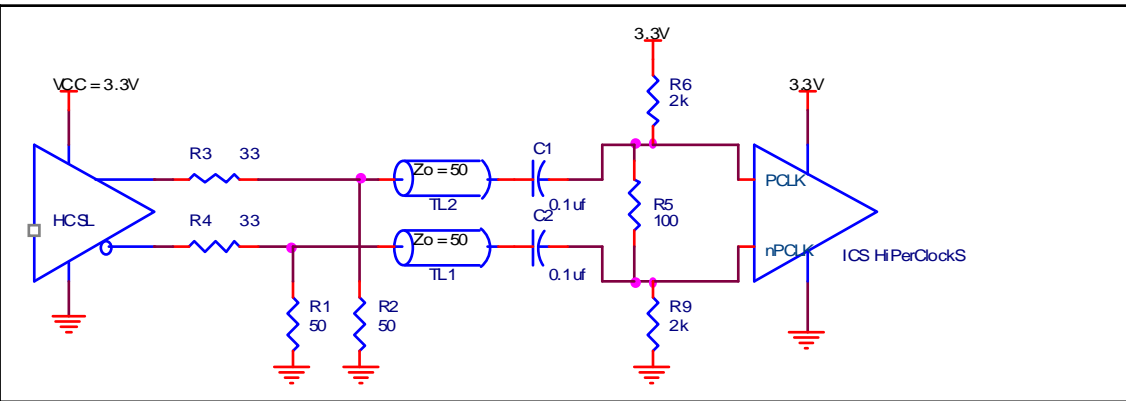


Figure 101. HCSL to IDT Differential PCLK/nPCLK, Option 3

 


Figure 102. HCSL to IDT Differential PCLK/nPCLK, Option 4


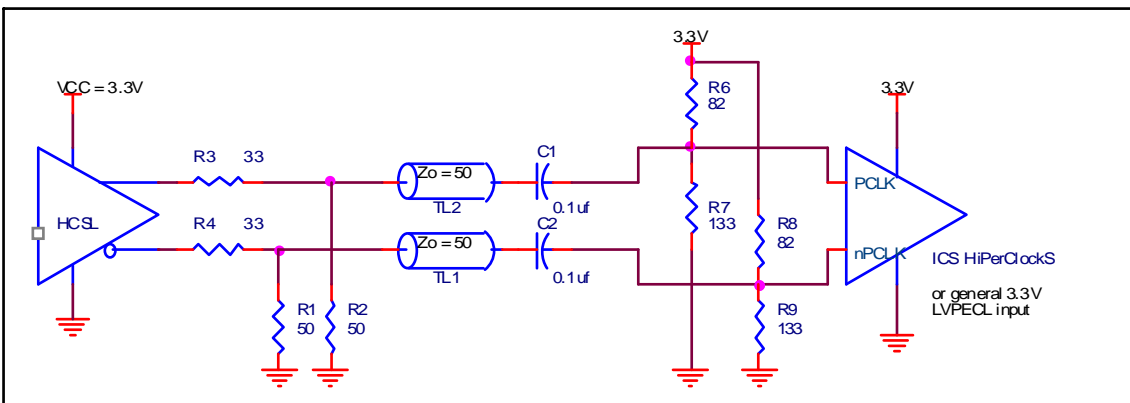


Figure 103. HCSL to 400mV Swing

 

Reduce R5/R6 values to further reduce the amplitude.

Figure 104. HCSL to 1.5V Differential HSTL Interface

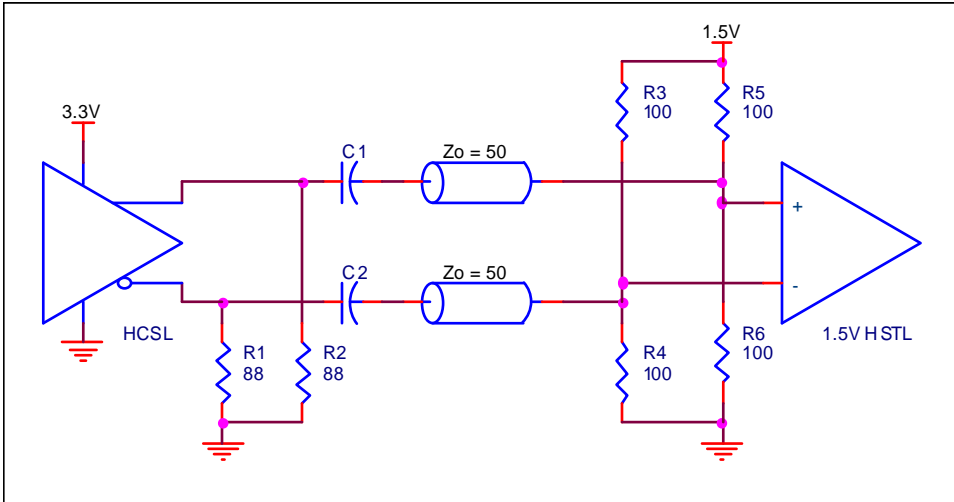


Figure 105. HCSL to 1.8V LVCMOS

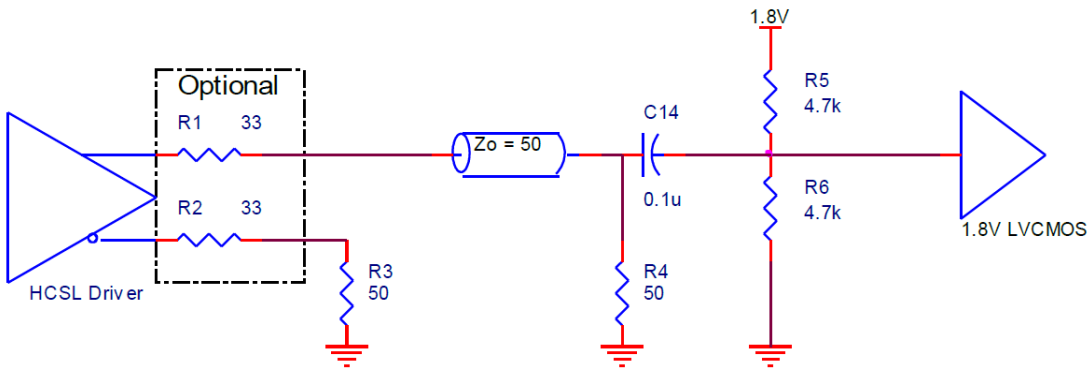


Figure 106. HCSL to Xilinx Vertex 5



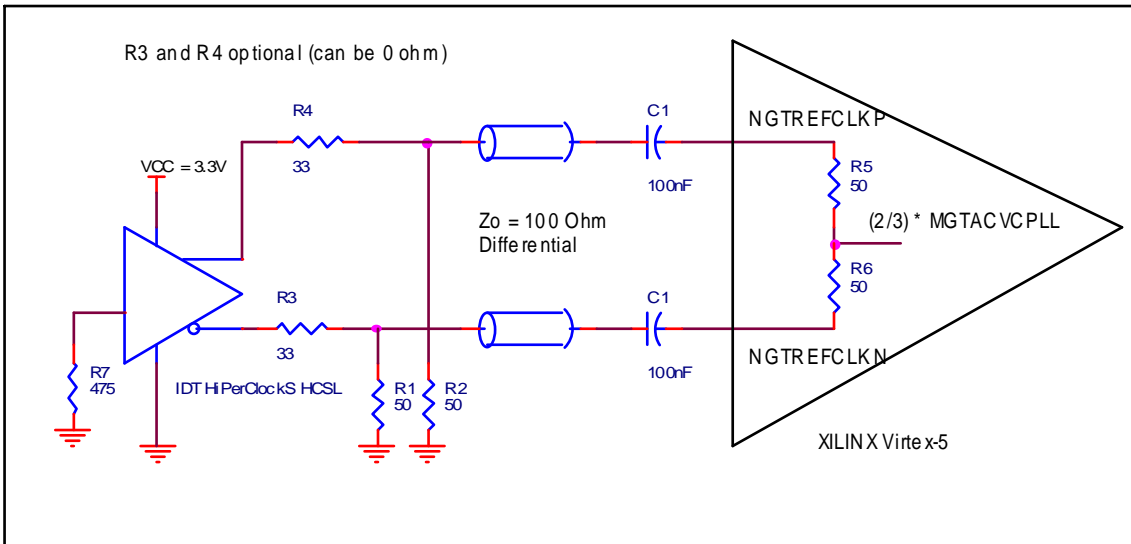


Figure 107. HCSL PCIe Source Termination

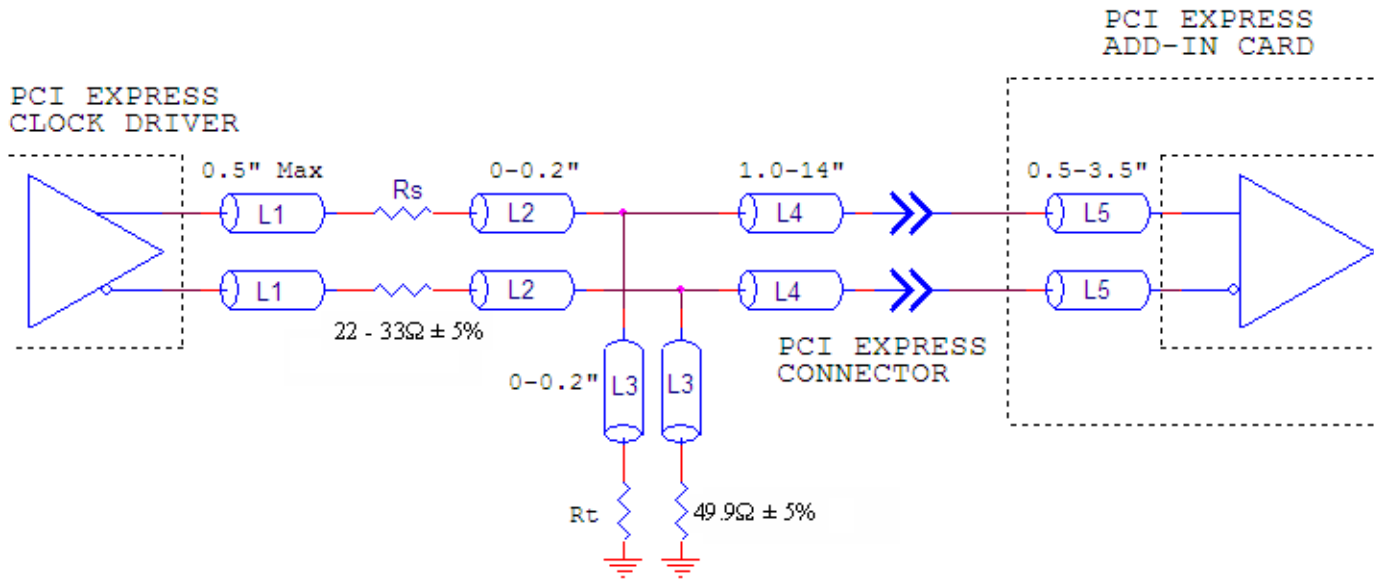

Recommended termination for applications which require the receiver and driver to be on a separate circuit board.

Figure 108. HCSL PCIe Receiver Termination

 

Recommended termination for applications which require a point to point connection and driver and receiver are on the same board.

CML Terminations

Figure 109. CML Standard Termination

 


Figure 110. CML to Differential CLK/nCLK

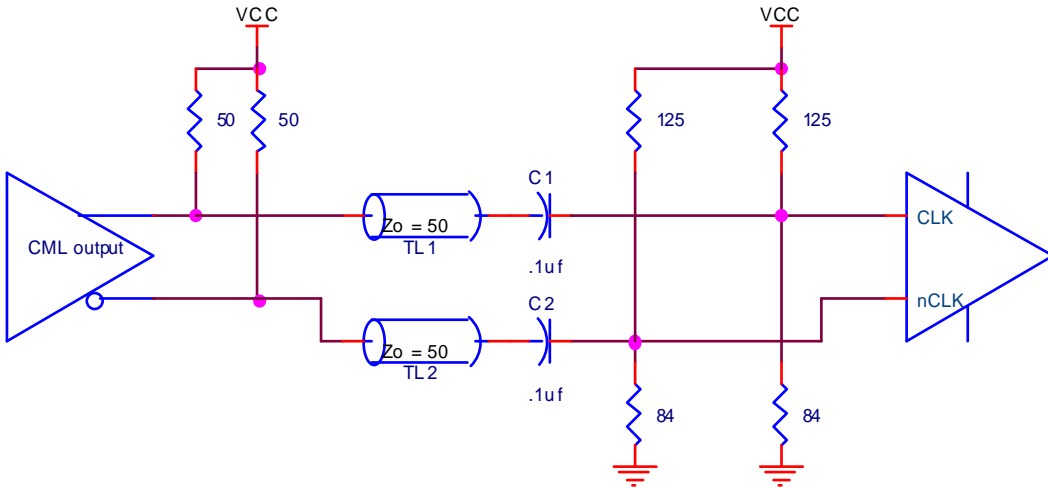


Figure 111. CML to HCSL - Receiver with High Input Impedance

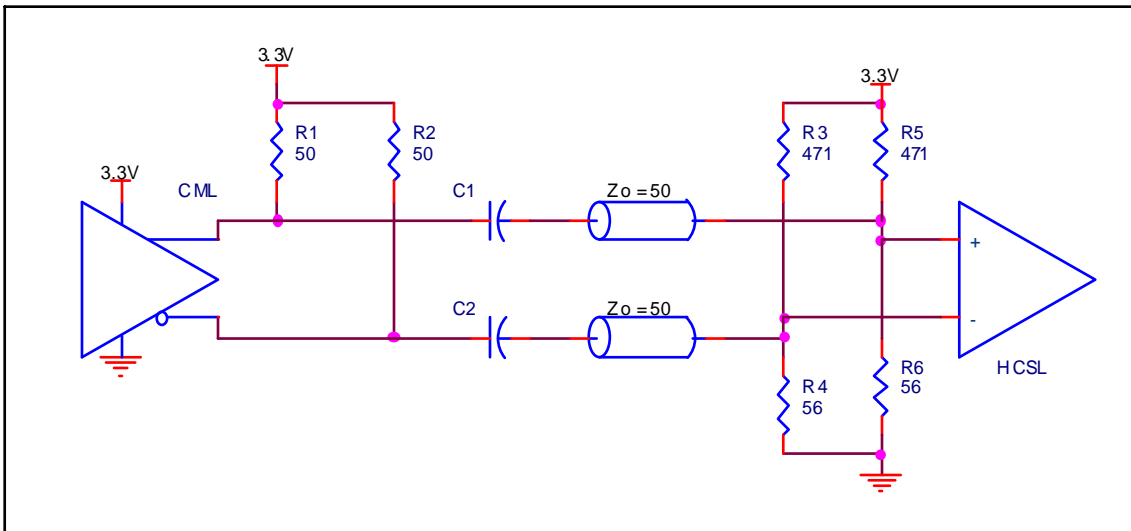


Figure 112. Receiver with Built-in 100 ohm Across


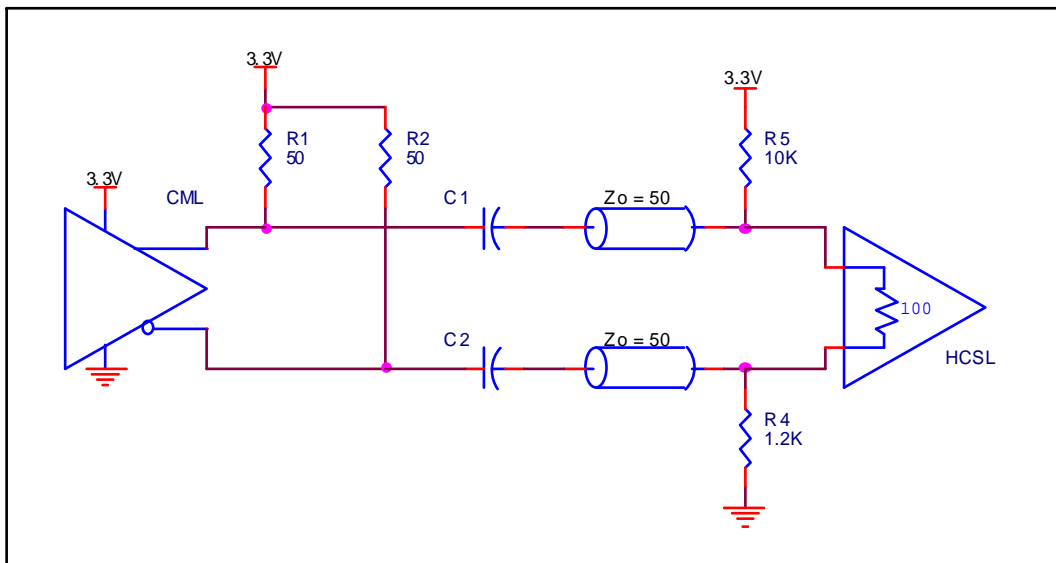


Figure 113. CML to HCSL - Receiver with Built-in 50 ohm to Ground

 

SSTL Terminations

Figure 114. SSTL 1.8V to Differential PCLK/nPCLK with VBB

 


Figure 115. SSTL 1.8V to Differential PCLK/nPCLK, Option 1

 


Figure 116. SSTL 1.8V to Differential PCLK/nPCLK, Option 2



 


Figure 117. SSTL 1.8V to Differential PCLK/nPCLK, Option 3

 

Low-Power- HCSL

Figure 118. Universal Network

 

The above schematic uses a LP-HCSL driver with integrated termination resistors (RS). When using a driver where the termination is not integrated, please add RS=33Ω in series with each pin externally to complete the driver output impedance to 50Ω.


Equations for [Figure 118](#)

The Common Mode Voltage depends upon RN, RP and VDD: $V_{CM} = VDD \times RN / (RN + RP)$

The following equation calculates the single-ended swing at the receiver input pins:

$$V_{SWING} = 800mV_{pp} \times (RN \parallel RP \parallel \frac{1}{2}RD) / (50 + RN \parallel RP \parallel \frac{1}{2}RD)$$

Figure 119. Universal Network with Amplitude Attenuation

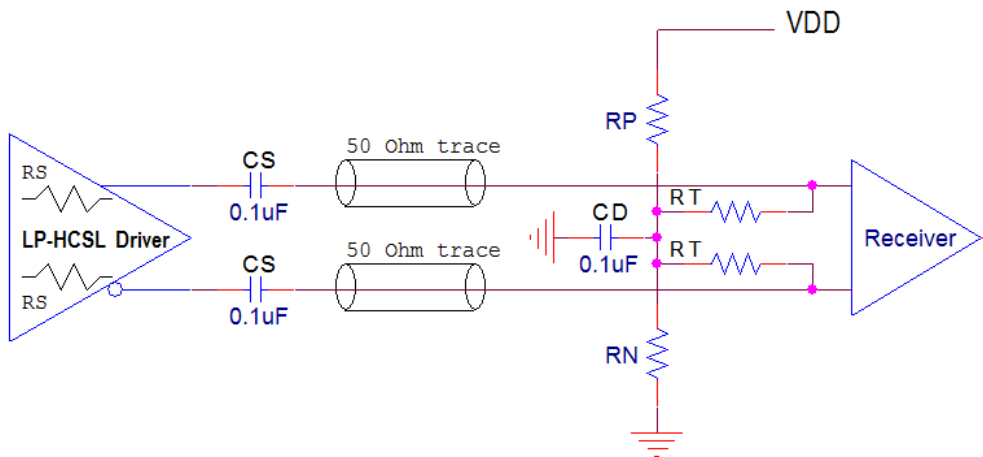


Equations for [Figure 119](#)

Common Mode Voltage: $V_{CM} = VDD \times RN / (RN + RP)$

Receiver Input Single-ended Voltage Swing: $V_{SWING} = 800mV_{pp} \times RT / (50 + RT)$

Rewriting to find RT for the required VSWING: $RT = 50 \times V_{SWING} / (800mV_{pp} - V_{SWING})$

Figure 120. Terminating LP-HCSL to LVPECL with Network

 


VDD	RP	RN	CS*	V _{SWING} **	V _{CM}
3.3V	2200Ω	3300Ω	0.1μF	771mVpp	1.98V
2.5V	2700Ω	2400Ω	0.1μF	770mVpp	1.18V

* Also add RS=33Ω in series when not integrated in the LP-HCSL driver.

** Single-ended voltage swing, based upon 800mVpp at the LP-HCSL driver.

Figure 121. Terminating LP-HCSL to LVDS without Integrated RD

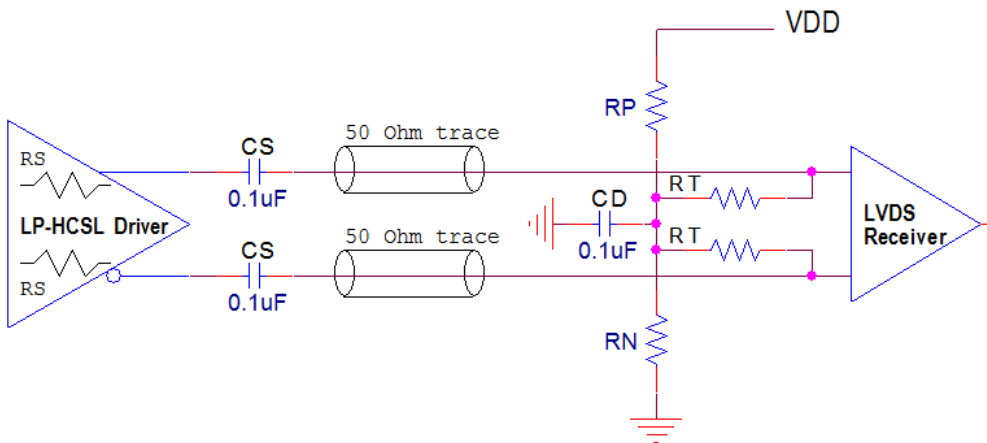


VDD	RP	RN	RT	CS*	CD**	V _{SWING} ***	V _{CM}
3.3V	3000Ω	1800Ω	50Ω	0.1μF	0.1μF	400mVpp	1.24V
2.5V	2200Ω	2200Ω	50Ω	0.1μF	0.1μF	400mVpp	1.25V
1.8V	1500Ω	3300Ω	50Ω	0.1μF	0.1μF	400mVpp	1.24V

* Also add RS=33Ω in series when not integrated in the LP-HCSL driver.

** CD is optional for filtering common mode noise in the clock.

*** Single-ended voltage swing, based upon 800mVpp at the LP-HCSL driver.


Figure 122. Terminating LP-HCSL to LVDS with Integrated RD

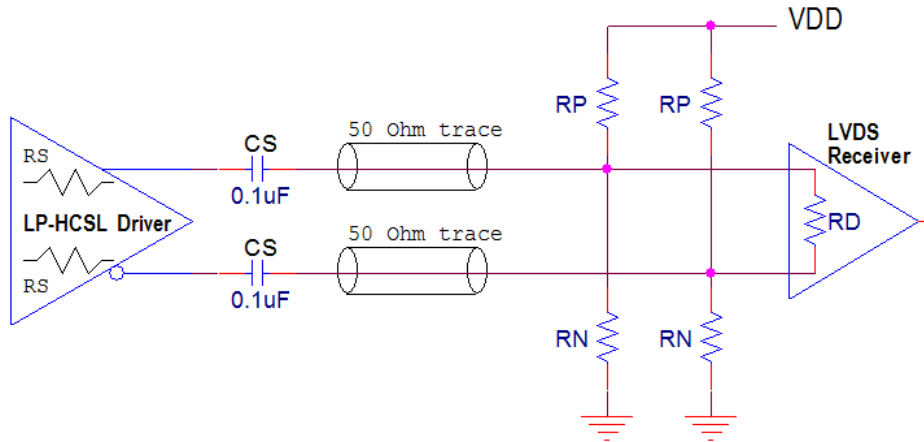

VDD	RP	RN	RD**	CS*	V _{SWING} ***	V _{CM}
3.3V	3000Ω	1800Ω	100Ω	0.1μF	391mVpp	1.24V
2.5V	2200Ω	2200Ω	100Ω	0.1μF	391mVpp	1.25V
1.8V	1500Ω	3300Ω	100Ω	0.1μF	391mVpp	1.24V

- * Also add RS=33Ω in series when not integrated in the LP-HCSL driver.
- ** RD is integrated in the receiver so we don't have to assemble it.
- *** Single-ended voltage swing, based upon 800mVpp at the LP-HCSL driver.


Figure 123. Terminating LP-HCSL to a CML Receiver

 

RT*	CS**	V _{SWING} ***	V _{CM} ****
50Ω	0.1μF	400mVpp	VDD


- * RT is only needed when not integrated in the CML receiver input.
- ** Also add RS=33Ω in series when not integrated in the LP-HCSL driver.
- *** Single ended voltage swing, based upon 800mVpp at the LP-HCSL driver.
- **** VDD is the value used for the CML receiver and does not need to be the same as for the LP-HCSL driver.

Figure 124. Terminating LP-HCSL to a Self-biasing Generic Receiver with On-chip Termination and AC-Coupling

 

In this case, we can connect the LP-HCSL output directly to the receiver input pins without any additional components. The swing at the receiver input is 400mVpp single ended or 800mVpp differential. Receivers often specify the swing differential.

Figure 125. Terminating LP-HCSL to a Generic Receiver with On-chip Termination

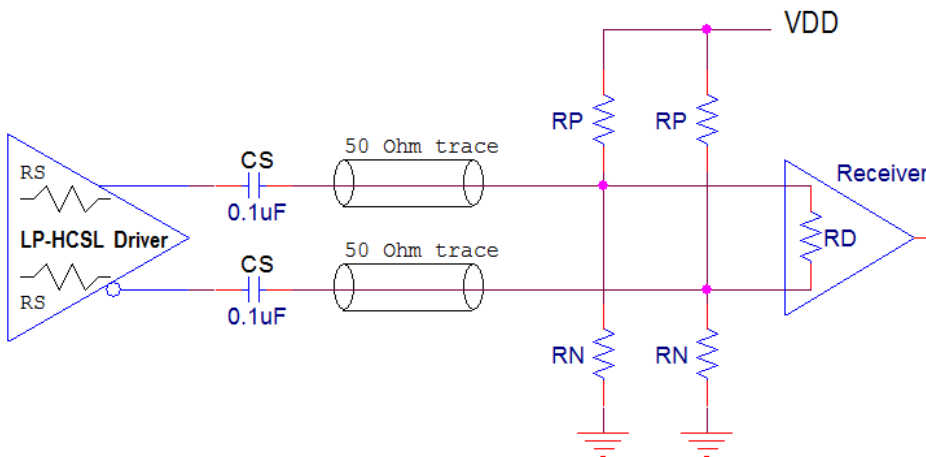


The receiver datasheet may recommend R_P and R_N values. If not, use the equation on page 2 to find R_P and R_N values for the required common mode voltage. Make sure that the resistance value for R_N and R_P in parallel is at least $1K\Omega$ to not load the signal lines too much.

When V_{DD} is for the receiver and the IC's datasheet does not specify a common mode voltage, a good V_{CM} value is $50\%V_{DD}$. In this case R_P and R_N can have the same value, for example 2200Ω each.

The swing at the receiver input is 391mVpp single ended with $R_N = R_P = 2200\Omega$.

Figure 126. Terminating LP-HCSL to Generic Receiver without Termination or Self-biasing

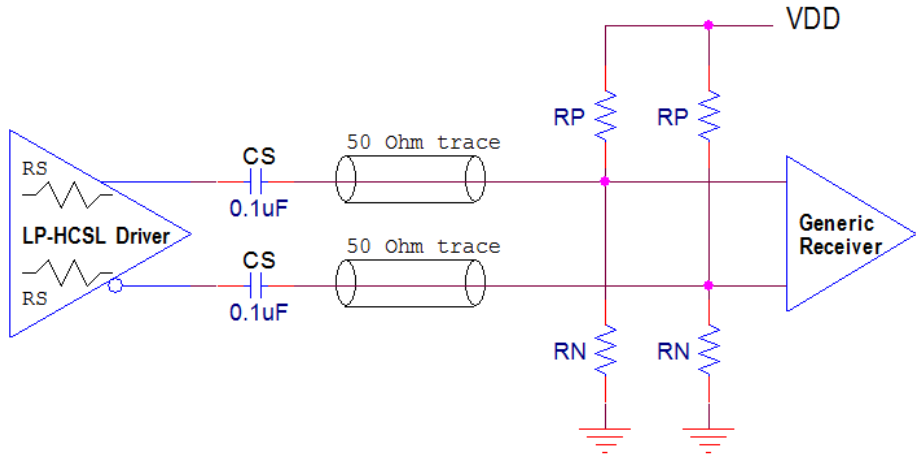

Because generic differential inputs can often handle up to 1000mVpp of swing at the input pins we do not need to attenuate. For noise reasons it is beneficial to make as large a swing as possible.

For RN and RP values, see the previous circuit for a differential input with on-chip termination

Revision History

Table 1. Revision History

Revision Date	Description of Change
March 6, 2017	▪ Updated legal disclaimer
December 9, 2016	▪ Initial release

Notice

1. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation or any other use of the circuits, software, and information in the design of your product or system. Renesas Electronics disclaims any and all liability for any losses and damages incurred by you or third parties arising from the use of these circuits, software, or information.
2. Renesas Electronics hereby expressly disclaims any warranties against and liability for infringement or any other claims involving patents, copyrights, or other intellectual property rights of third parties, by or arising from the use of Renesas Electronics products or technical information described in this document, including but not limited to, the product data, drawings, charts, programs, algorithms, and application examples.
3. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
4. You shall not alter, modify, copy, or reverse engineer any Renesas Electronics product, whether in whole or in part. Renesas Electronics disclaims any and all liability for any losses or damages incurred by you or third parties arising from such alteration, modification, copying or reverse engineering.
5. Renesas Electronics products are classified according to the following two quality grades: "Standard" and "High Quality". The intended applications for each Renesas Electronics product depends on the product's quality grade, as indicated below.
 - "Standard": Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; industrial robots; etc.
 - "High Quality": Transportation equipment (automobiles, trains, ships, etc.); traffic control (traffic lights); large-scale communication equipment; key financial terminal systems; safety control equipment; etc.Unless expressly designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not intended or authorized for use in products or systems that may pose a direct threat to human life or bodily injury (artificial life support devices or systems; surgical implantations; etc.), or may cause serious property damage (space system; undersea repeaters; nuclear power control systems; aircraft control systems; key plant systems; military equipment; etc.). Renesas Electronics disclaims any and all liability for any damages or losses incurred by you or any third parties arising from the use of any Renesas Electronics product that is inconsistent with any Renesas Electronics data sheet, user's manual or other Renesas Electronics document.
6. When using Renesas Electronics products, refer to the latest product information (data sheets, user's manuals, application notes, "General Notes for Handling and Using Semiconductor Devices" in the reliability handbook, etc.), and ensure that usage conditions are within the ranges specified by Renesas Electronics with respect to maximum ratings, operating power supply voltage range, heat dissipation characteristics, installation, etc. Renesas Electronics disclaims any and all liability for any malfunctions, failure or accident arising out of the use of Renesas Electronics products outside of such specified ranges.
7. Although Renesas Electronics endeavors to improve the quality and reliability of Renesas Electronics products, semiconductor products have specific characteristics, such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Unless designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not subject to radiation resistance design. You are responsible for implementing safety measures to guard against the possibility of bodily injury, injury or damage caused by fire, and/or danger to the public in the event of a failure or malfunction of Renesas Electronics products, such as safety design for hardware and software, including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult and impractical, you are responsible for evaluating the safety of the final products or systems manufactured by you.
8. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. You are responsible for carefully and sufficiently investigating applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive, and using Renesas Electronics products in compliance with all these applicable laws and regulations. Renesas Electronics disclaims any and all liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
9. Renesas Electronics products and technologies shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations. You shall comply with any applicable export control laws and regulations promulgated and administered by the governments of any countries asserting jurisdiction over the parties or transactions.
10. It is the responsibility of the buyer or distributor of Renesas Electronics products, or any other party who distributes, disposes of, or otherwise sells or transfers the product to a third party, to notify such third party in advance of the contents and conditions set forth in this document.
11. This document shall not be reprinted, reproduced or duplicated in any form, in whole or in part, without prior written consent of Renesas Electronics.
12. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products.

(Note1) "Renesas Electronics" as used in this document means Renesas Electronics Corporation and also includes its directly or indirectly controlled subsidiaries.

(Note2) "Renesas Electronics product(s)" means any product developed or manufactured by or for Renesas Electronics.

(Rev.4.0-1 November 2017)

Corporate Headquarters

TOYOSU FORESIA, 3-2-24 Toyosu,
Koto-ku, Tokyo 135-0061, Japan
www.renesas.com

Contact Information

For further information on a product, technology, the most up-to-date version of a document, or your nearest sales office, please visit:
www.renesas.com/contact/

Trademarks

Renesas and the Renesas logo are trademarks of Renesas Electronics Corporation. All trademarks and registered trademarks are the property of their respective owners.