

## Introduction

IDT's Low-Power (LP) HCSL drivers (often referred to as push-pull HCSL, or PCIe drivers) can easily drive a variety of other logic types, in addition to HCSL. A simple, passive network can adjust the swing and common mode voltage to required levels. The LP-HCSL driver can be viewed as a low-power 0~800mV square wave generator terminated to 50Ω output impedance. It can be used to drive any other logic that requires a swing of 800mVpp or less. With the driver source-terminated to 50Ω, receiver input terminations are not necessary; yet it is okay if the receiver is also terminated.

Note that we will adopt the convention of referring to the output impedance in a single-ended manner in this application note. A 100Ω differential impedance transmission line can be treated as 2 single-ended transmission lines of 50Ω for termination purposes.

Generic differential inputs can handle a wider range of differential swing and common mode voltages than standard logic families and are becoming more popular. This application note describes how to use LP-HCSL outputs to drive various standard logic types and the newer generic differential inputs. For additional information on LP-HCSL outputs, see IDT application note "[AN-879 Low-Power HCSL vs. Traditional HCSL](#)" at [www.idt.com](http://www.idt.com).

## Network Overview

Figure 1. Universal Network

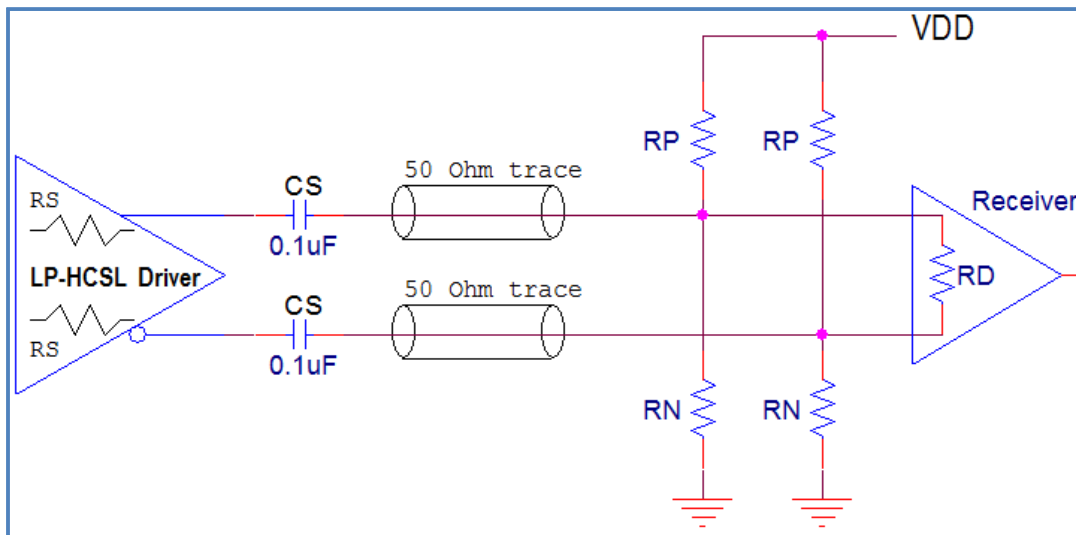


Figure 1 is a schematic of a universal differential clock network. Terminations for each logic type use a subset of this network, and the following paragraphs provide details.

The above schematic uses an LP-HCSL driver with integrated termination resistors (RS). When using a driver where the termination is not integrated, please add an external RS=33Ω in series with each pin to terminate the driver output impedance to 50Ω. Any external RS should be as close to the driver as possible and be between the driver and any AC coupling capacitor. This allows maximum flexibility in placement of the AC Coupling capacitors along the transmission line. Because the driver side is properly terminated, it is not necessary to terminate at the receiver side. For the receiver side we can focus on creating the proper signal swing and common mode voltage.

CS provides AC coupling so only the signal swing passes to the receiver. RP and RN will re-bias the signal's common mode voltage for the receiver. RP and RN can also attenuate signal swing when smaller resistor values are chosen. This increases the DC current in the network, and if this is unacceptable, an alternative network shown in Figure 2 is recommended.

Some receivers use an integrated differential termination, represented by RD. If RD is integrated in the receiver, we need to include the RD value when calculating the RP and RN values. The most common value for an integrated RD is 100Ω.

VDD in Figure 1 does not need to be the same VDD value as for the LP-HCSL driver or the Receiver; however RP and RN are assembled near the receiver input, it is usually most convenient to use the receiver VDD.

**Equations for Figure 1:**

The Common Mode Voltage depends upon RN, RP and VDD:  $V_{CM} = VDD \times RN / (RN + RP)$

The receiver input signal swing depends upon the additional loading of RN, RP and RD at the receiver input. When RN and RP are much larger than 50Ω and there is no RD, the single-ended swing at the receiver input will be close to the 800mVpp at the driver. When RP and RN in parallel is 50Ω or RD=100Ω is present, the single-ended swing will attenuate to 400mVpp.

The following equation calculates the single-ended swing at the receiver input pins:

$$V_{SWING} = 800mVpp \times (RN \parallel RP \parallel \frac{1}{2}RD) / (50 + RN \parallel RP \parallel \frac{1}{2}RD)$$

"//" means "parallel to". This equation assumes a differential signal with equal but opposite waveforms at the two pins of the receiver. The equation can be simplified to the following:

$$V_{SWING} = 800mVpp \times RN \times RP \times RD / (RN \times RP \times RD + 50 \times RN \times RD + 50 \times RP \times RD + 100 \times RN \times RP)$$

When RD=100Ω:  $V_{SWING} = 800mVpp \times RN \times RP / (2 \times RN \times RP + 50 \times RN + 50 \times RP)$

When there is no RD:  $V_{SWING} = 800mVpp \times RN \times RP / (RN \times RP + 50 \times RN + 50 \times RP)$

Receivers often specify the required input voltage swing as a differential value. The differential value is two times the single-ended value, so for a differential VSWING you can multiply the single-ended VSWING by 2.

**Figure 2. Universal Network with Amplitude Attenuation**

 


Figure 2 shows a slightly modified Universal Network that is most suitable when amplitude attenuation is required and/or reduced DC current is desired. Instead of choosing small values for RP and RN to provide the attenuation as required by the network shown in Figure 1, you can use the RT resistors as a differential load to provide the attenuation. RP and RN can have larger values to limit the DC current in the network.

CD is optional and can help balance the differential waveform at the receiver input. Essentially, CD filters common mode noise that may be present in the clock signal.

**Equations for Figure 2:**

Common Mode Voltage:  $V_{CM} = VDD \times RN / (RN + RP)$


Receiver Input Single-ended Voltage Swing:  $V_{SWING} = 800mVpp \times RT / (50 + RT)$

Rewriting to find RT for the required VSWING:  $RT = 50 \times V_{SWING} / (800mVpp - V_{SWING})$

### Driving LVPECL

LVPECL needs the full 800mVpp swing, so RP and RN set the common mode voltage while causing as little swing attenuation as possible.

**Figure 3. Terminating LP-HCSL to LVPECL with Network from Figure 1**

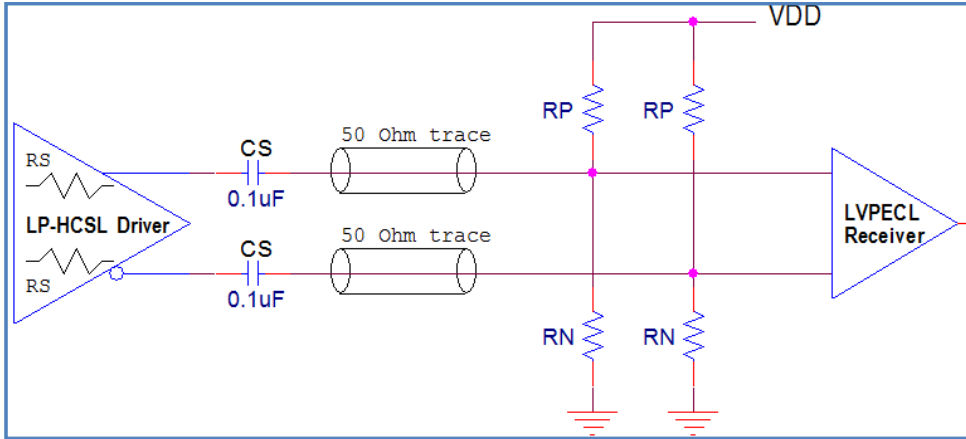


VDD	RP	RN	CS*	V <sub>SWING</sub> **	V <sub>CM</sub>
3.3V	2200Ω	3300Ω	0.1μF	771mVpp	1.98V
2.5V	2700Ω	2400Ω	0.1μF	770mVpp	1.18V

\* Also add RS=33Ω in series when not integrated in the LP-HCSL driver.

\*\* Single-ended voltage swing, based upon 800mVpp at the LP-HCSL driver

Figure 4 shows the measured waveform for the network in Figure 3 with VDD = 2.5V


**Figure 4. Measured Waveform at LVPECL Receiver with VDD=2.5V**

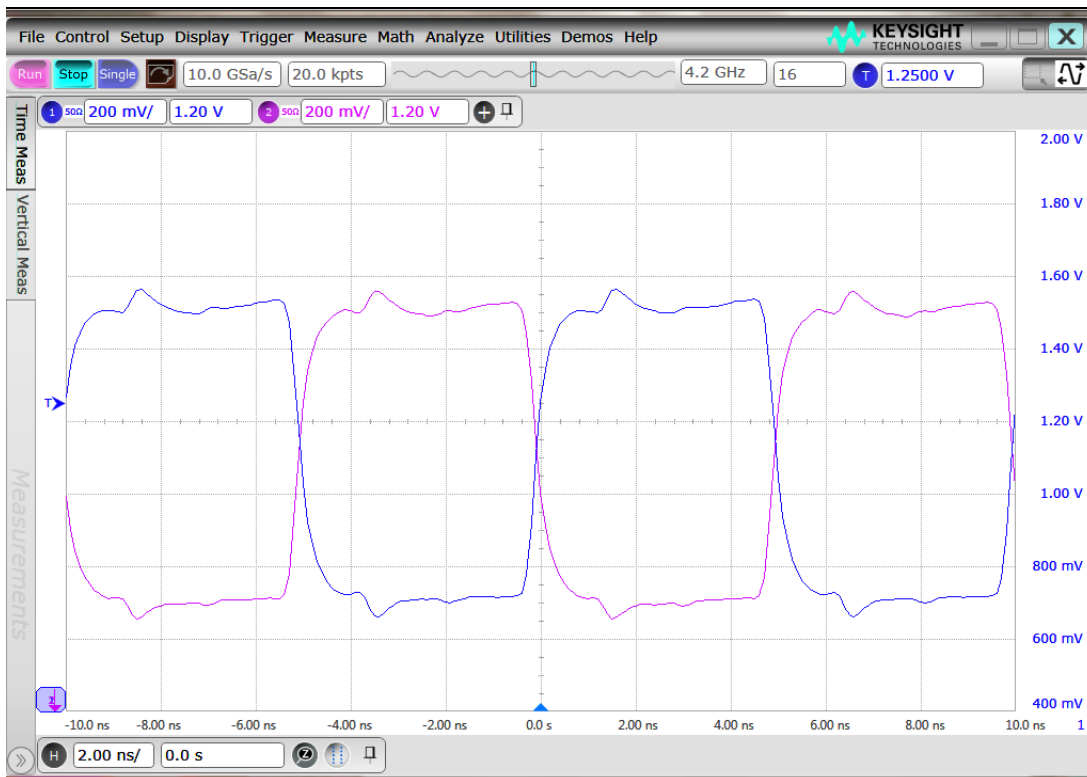

## Driving LVDS

LVDS needs 350~400mVpp single-ended swing at each input pin and a common mode voltage of 1.25V. Since LVDS requires both attenuation and a common mode voltage shift, we use the alternate circuit from [Figure 2](#):

**Figure 5. Terminating LP-HCSL to LVDS without Integrated RD**

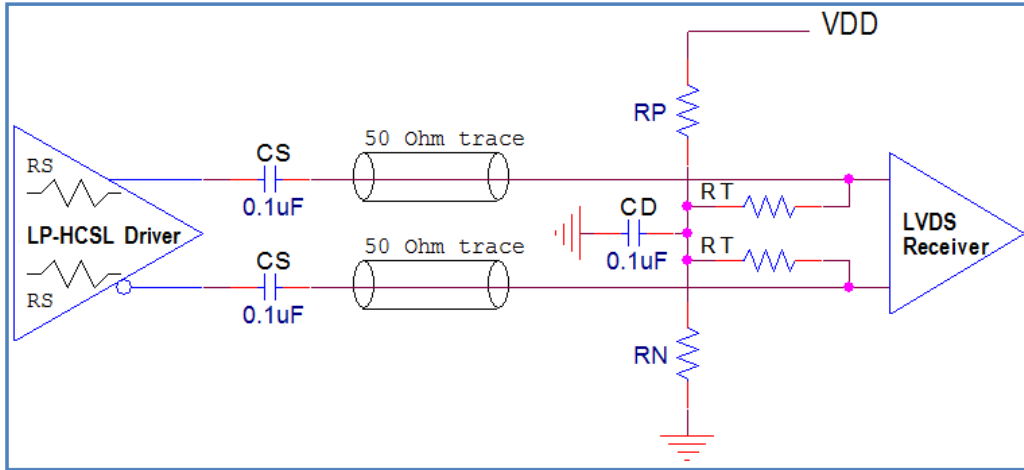

VDD	RP	RN	RT	CS*	CD**	V <sub>SWING</sub> ***	V <sub>CM</sub>
3.3V	3000Ω	1800Ω	50Ω	0.1μF	0.1μF	400mVpp	1.24V
2.5V	2200Ω	2200Ω	50Ω	0.1μF	0.1μF	400mVpp	1.25V
1.8V	1500Ω	3300Ω	50Ω	0.1μF	0.1μF	400mVpp	1.24V


\* Also add RS=33Ω in series when not integrated in the LP-HCSL driver.

\*\* CD is optional for filtering common mode noise in the clock.

\*\*\* Single-ended voltage swing, based upon 800mVpp at the LP-HCSL driver.

If the LVDS receiver has an on-chip differential termination resistor (RD=100Ω), re-biasing is not necessary and [Figure 1](#) can be used.

**Figure 6. Terminating LP-HCSL to LVDS with Integrated RD**

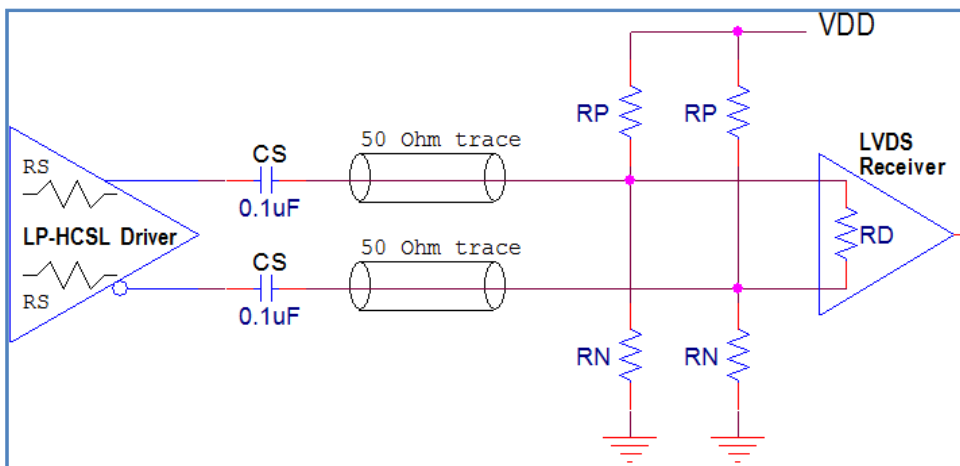

VDD	RP	RN	RD**	CS*	V <sub>SWING</sub> ***	V <sub>CM</sub>
3.3V	3000Ω	1800Ω	100Ω	0.1μF	391mVpp	1.24V
2.5V	2200Ω	2200Ω	100Ω	0.1μF	391mVpp	1.25V
1.8V	1500Ω	3300Ω	100Ω	0.1μF	391mVpp	1.24V


\* Also add RS=33Ω in series when not integrated in the LP-HCSL driver.

\*\* RD is integrated in the receiver so we don't have to assemble it.

\*\*\* Single-ended voltage swing, based upon 800mVpp at the LP-HCSL driver

Figure 7 shows the measured waveform for the network shown in Figure 6:


Figure 7. Measured Waveform at LVDS Receiver

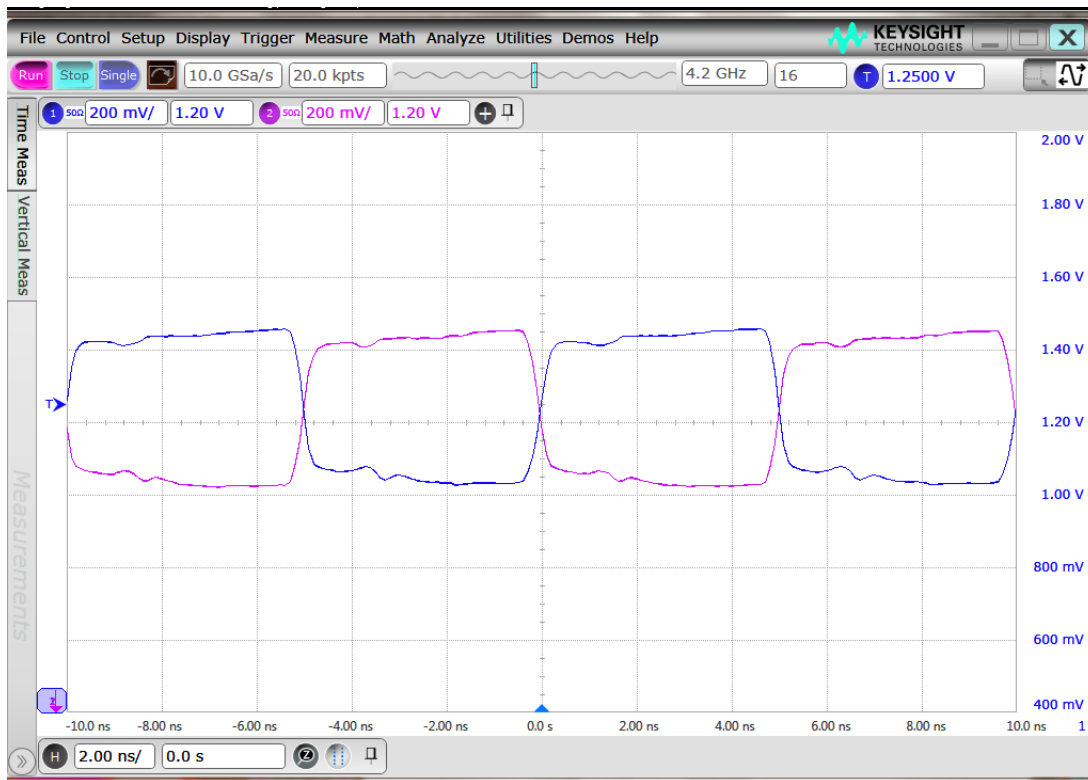

## Driving CML

CML uses termination resistors connected to VDD at the receiver input. CML needs a single-ended signal swing of 400mVpp and allows the clock to be AC coupled. This means that we do not need to provide a common mode voltage which simplifies the network.

**Figure 8. Terminating LP-HCSL to a CML Receiver**

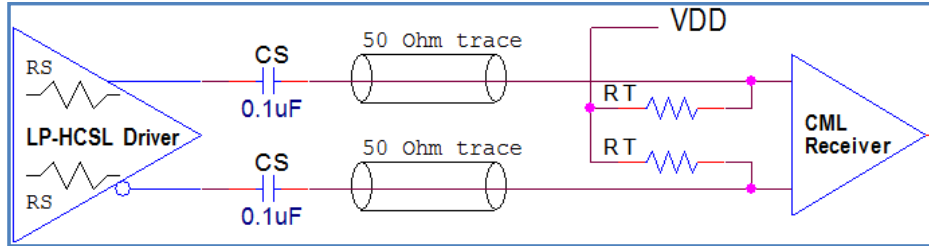

RT	CS*	V <sub>SWING</sub> **	V <sub>CM</sub> ***
50Ω	0.1μF	400mVpp	VDD

\* Also add RS=33Ω in series when not integrated in the LP-HCSL driver.


\*\* Single-ended voltage swing, based upon 800mVpp at the LP-HCSL driver.

\*\*\* VDD is the value used for the CML receiver and does not need to be the same as for the LP-HCSL driver.

If the CML receiver has on-chip termination resistors, we can omit the RT resistors.

Figure 9 shows the measured waveform for the network shown in Figure 8.

**Figure 9. Measured Waveform at CML Receiver**

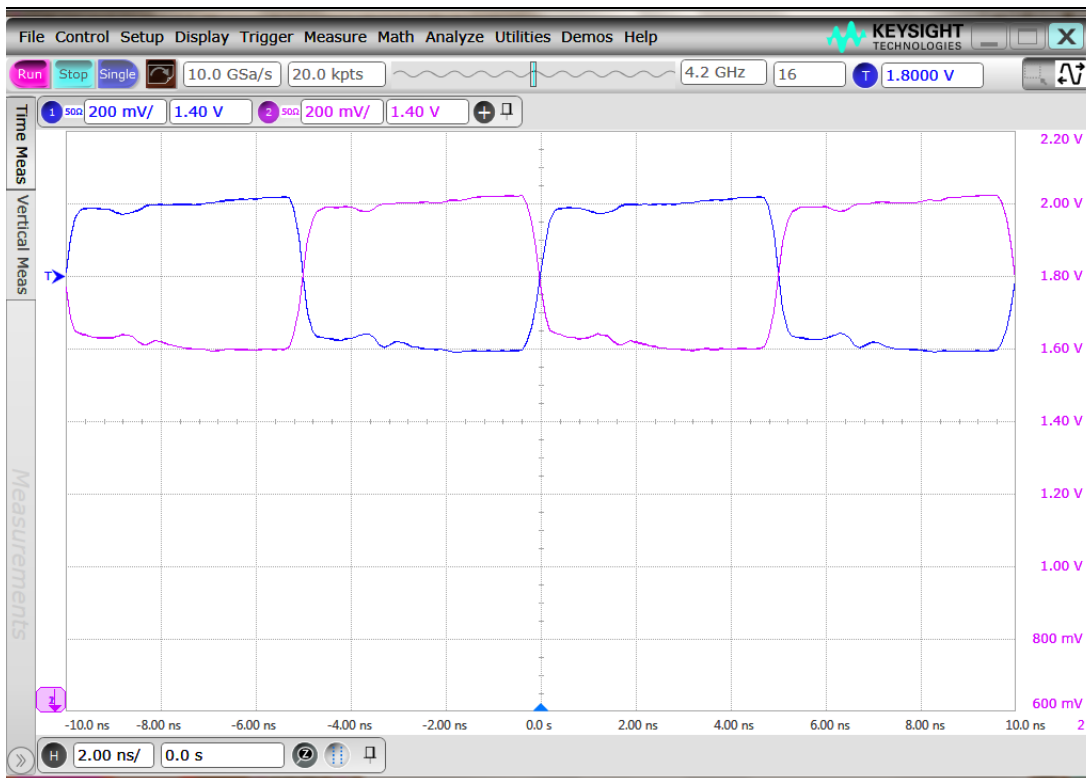

## Driving SSTL

SSTL signaling is commonly used with DDR memory. SSTL drivers are similar to TTL and CMOS drivers with the exception that SSTL is differential. An SSTL differential input resembles an LVDS or CML input, and can handle large signal swings of up to 0.3V outside the power rails, or small signal swings down to a few hundred millivolts peak-to-peak.

The typical SSTL-driver-to-SSTL-receiver connection is terminated at both the driver side and the receiver side. So, a rail-to-rail swing at the driver will result in a  $0.5 \times V_{DD}$  peak-to-peak swing at the receiver.


LP-HCSL drivers can drive SSTL receiver inputs. When terminating on both the LP-HCSL driver side and the SSTL receiver side, the typical signal swing at the SSTL receiver input will be 400mVpp. This is enough swing for SSTL-15 (1.5V, DDR3) and SSTL-135 (1.35V, DDR3L). See JESD82-29A for additional DDR3(L) requirements. SSTL-18 (1.8V, DDR2) needs a swing of at least 500mVpp according to JESD8-15A.

When driving actual DDR memory, it is best to follow the JEDEC spec numbers. FPGAs with SSTL compatible inputs can often handle smaller clock signal amplitudes. Please consult the FPGA datasheet for actual clock signal amplitude requirements. For SSTL-18 (DDR2) we can achieve the required amplitude by eliminating the source termination at the LP-HCSL driver side and use only the end termination at the SSTL receiver side. This requires an LP-HCSL driver that does not have the internal termination. With this single termination approach the clock amplitude at the SSTL receiver input reaches 600mVpp.

Logic	VDD1	Application	JEDEC	AC V <sub>swing</sub> Requirement*
SSTL_18	1.8V	DDR2	JESD8-15A	500mVpp
SSTL_15	1.5V	DDR3	JESD82-29A	350mVpp
SSTL_135	1.35V	DDR3L	JESD82-29A	300mVpp

\* The AC Swing requirement is a larger value than the DC Swing requirement because it includes a margin for noise. When driving a SSTL compatible input on an FPGA, the Swing requirement may be a lower value.


**Figure 10. Recommended Circuit for SSTL-15 and SSTL-135**

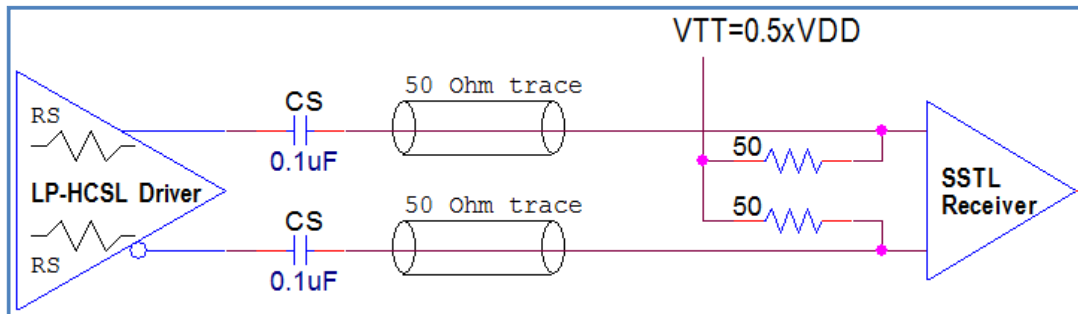

VTT is a reference voltage of  $0.5 \times V_{DD}$  that is available with DDR circuits.

In case VTT is not available, the following alternative termination can be used:


**Figure 11. Recommended Circuit for SSTL-15 and SSTL-135 when VTT is not available**

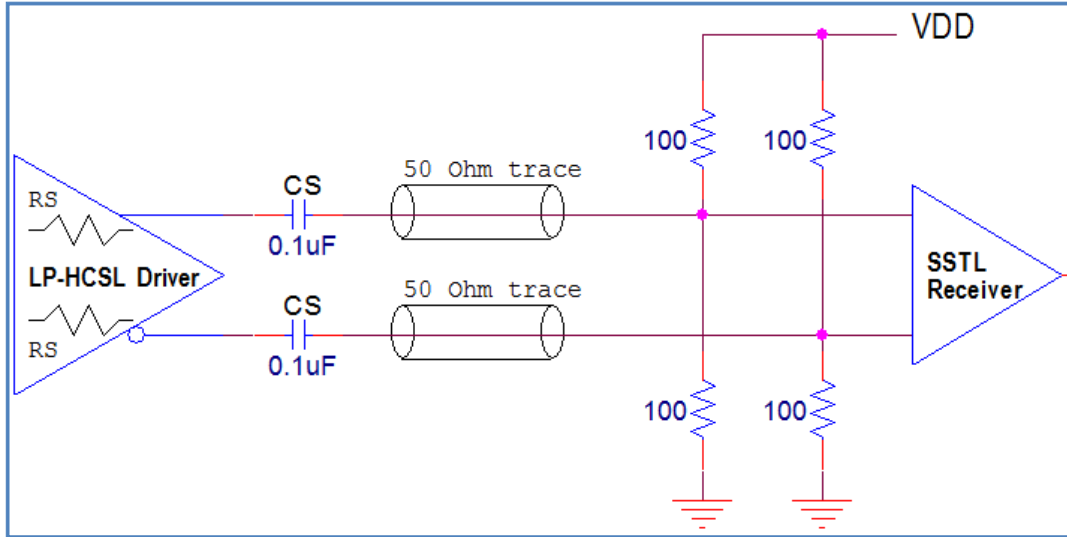

VDD in both circuits is the VDD of the SSTL receiver. In SSTL or DDR documentation this VDD is often referred to as VDDQ.

For the SSTL-18 (DDR2) case that requires at least 500mVpp of clock signal swing, please use a LP-HCSL driver that does not have internal termination.

**Figure 12. Recommended Circuit for SSTL-18, using a LP-HCSL Driver without Internal Termination**

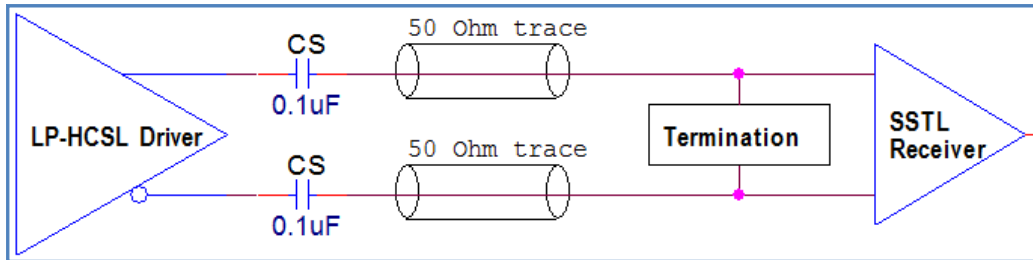


The same end terminations as in [Figure 10](#) and [Figure 11](#) can be used with the circuit in [Figure 12](#). The circuits in [Figure 10](#) and [Figure 11](#) are both source and end-terminated, the circuit in [Figure 12](#) is only end-terminated. The LP-HCSL driver without internal termination has an output impedance of 17Ω. The attenuation with the end termination is now  $50 / (17+50) = 0.75\times$ . Starting with 800mVpp HCSL amplitude, the amplitude at the receiver input is reduced to  $0.75 \times 800 = 600\text{mVpp}$ . The situation is similar to LVPECL where you also drive 50Ω traces with a low impedance driver. The proper 50Ω termination at the end prevents reflections and preserves signal integrity.

FPGAs may have SSTL compatible inputs with the termination on the chip. In that case the external termination at the SSTL receiver input can be removed and all that's left is the AC coupling capacitors. Also see the section "Driving Generic Differential Inputs".



Figure 13. Recommended Circuit for SSTL Compatible Inputs on an FPGA

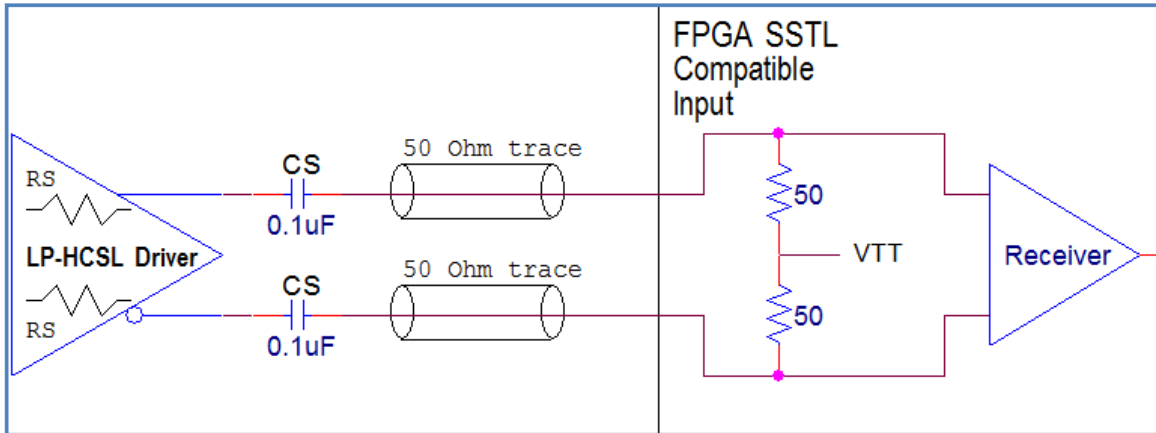


FPGAs often can work with much smaller signal amplitudes at the receiver input than with a standard SSTL input and this circuit can work with many SSTL types.

## Driving Generic Differential Inputs


More ICs are using generic differential receivers, often with an on-chip differential termination resistor. While compatible with LVDS, such devices commonly accept larger signal swings than specified for LVDS. For example, FPGAs commonly have on-chip receiver terminations and require LVDS signal swings at a minimum, while specifying a different common mode voltage. The FPGA datasheet may have a network like that shown in Figure 1 and will recommend values for  $R_P$  and  $R_N$ . Below are recommended circuits for driving a variety of generic receiver inputs.

**Figure 14. Terminating LP-HCSL to a Self-biasing Generic Receiver with On-chip Termination and AC-Coupling**

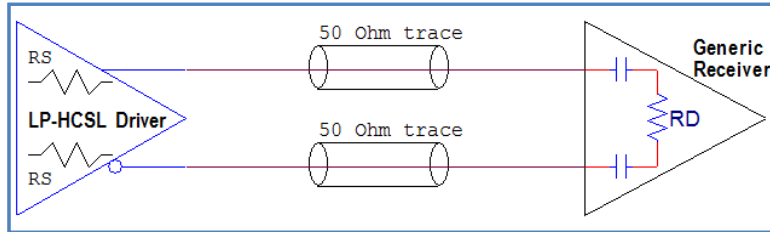

Refer to Figure 14. In this case all we need is  $R_S$  and, when  $R_S$  is integrated, we can connect the LP-HCSL output directly to transmission line without any additional components. The swing at the receiver input is 400mVpp single-ended or 800mVpp differential. Note, receivers often specify the swing differentially.

**Figure 15. Terminating LP-HCSL to a Generic Receiver with On-chip Termination**

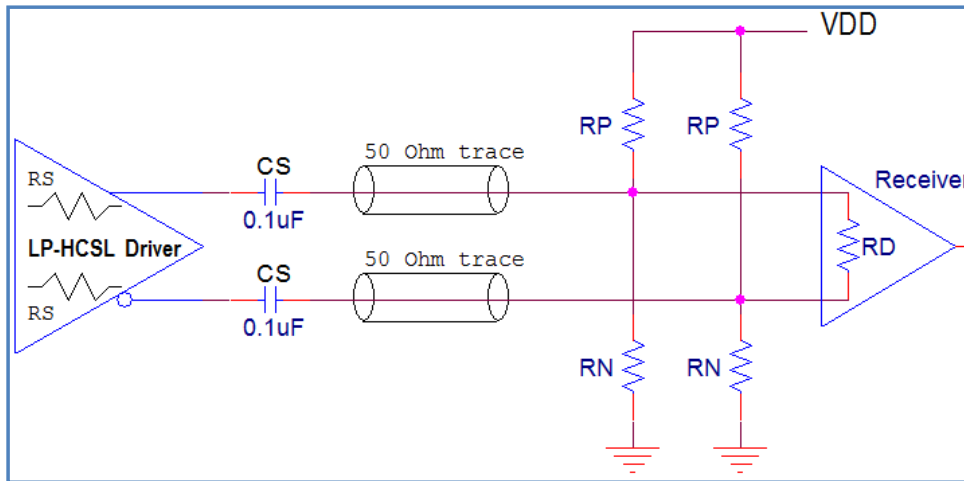


Refer to Figure 15. The receiver datasheet may recommend  $R_P$  and  $R_N$  values. If not, use the equation on page 1 to find  $R_P$  and  $R_N$  values for the required common mode voltage. Make sure that the resistance value for  $R_N$  and  $R_P$  in parallel is at least 1K $\Omega$  to minimize DC current in the termination network.

When VDD is the same value as the receiver VDD, and the IC's datasheet does not specify a common mode voltage, a good VCM value is 50%VDD. In this case  $R_P$  and  $R_N$  can have the same value, for example 2200 $\Omega$  each.

The swing at the receiver input is then 391mVpp single-ended for  $R_N = R_P = 2200\Omega$ .

**Figure 16. Terminating LP-HCSL to Generic Receiver without Termination or Self-biasing**

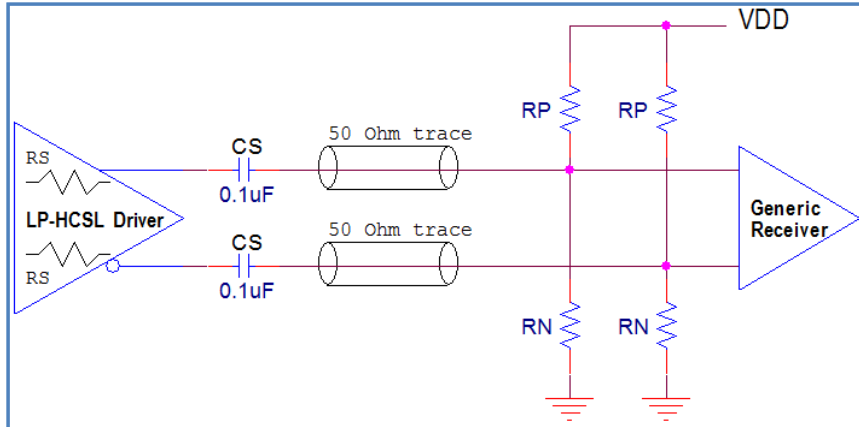

Refer to [Figure 16](#). Generic differential receivers can often handle up to 1000mVpp of swing (single-ended) at the input pins. For these receivers attenuation is not needed and it is beneficial to keep the swing as large as possible. For RN and RP values, see the previous circuit for a differential input with on-chip termination.

### 85-ohm Differential Trace Impedances

Many systems use 42.5Ω single-ended (or 85Ω differential) trace impedances and IDT offers LP-HCSL devices with integrated RS for these systems, as well. The equations in this application note apply to 85 ohm systems with minor changes to resistor and impedance values. The 50 ohm trace becomes a 42.5 ohm trace. This changes the RS value from 33 ohms to  $[33 - (50 - 42.5)]\text{ohms} = (33 - 7.5)\text{ ohms} = 25.5\text{ ohms}$  for 1% resistors. If 5% resistors are desired, RS becomes 24 ohms.

### Conclusion

Low-power HCSL drivers can be used as a generic differential driver for a wide variety of differential input types. At the same time LP-HCSL can use up to 9x less power than traditional HCSL drivers, and up to 19x less power than LVPECL, LVDS or CML drivers.



## Notice

1. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation or any other use of the circuits, software, and information in the design of your product or system. Renesas Electronics disclaims any and all liability for any losses and damages incurred by you or third parties arising from the use of these circuits, software, or information.
2. Renesas Electronics hereby expressly disclaims any warranties against and liability for infringement or any other claims involving patents, copyrights, or other intellectual property rights of third parties, by or arising from the use of Renesas Electronics products or technical information described in this document, including but not limited to, the product data, drawings, charts, programs, algorithms, and application examples.
3. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
4. You shall not alter, modify, copy, or reverse engineer any Renesas Electronics product, whether in whole or in part. Renesas Electronics disclaims any and all liability for any losses or damages incurred by you or third parties arising from such alteration, modification, copying or reverse engineering.
5. Renesas Electronics products are classified according to the following two quality grades: "Standard" and "High Quality". The intended applications for each Renesas Electronics product depends on the product's quality grade, as indicated below.
  - "Standard": Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; industrial robots; etc.
  - "High Quality": Transportation equipment (automobiles, trains, ships, etc.); traffic control (traffic lights); large-scale communication equipment; key financial terminal systems; safety control equipment; etc.Unless expressly designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not intended or authorized for use in products or systems that may pose a direct threat to human life or bodily injury (artificial life support devices or systems; surgical implantations; etc.), or may cause serious property damage (space system; undersea repeaters; nuclear power control systems; aircraft control systems; key plant systems; military equipment; etc.). Renesas Electronics disclaims any and all liability for any damages or losses incurred by you or any third parties arising from the use of any Renesas Electronics product that is inconsistent with any Renesas Electronics data sheet, user's manual or other Renesas Electronics document.
6. When using Renesas Electronics products, refer to the latest product information (data sheets, user's manuals, application notes, "General Notes for Handling and Using Semiconductor Devices" in the reliability handbook, etc.), and ensure that usage conditions are within the ranges specified by Renesas Electronics with respect to maximum ratings, operating power supply voltage range, heat dissipation characteristics, installation, etc. Renesas Electronics disclaims any and all liability for any malfunctions, failure or accident arising out of the use of Renesas Electronics products outside of such specified ranges.
7. Although Renesas Electronics endeavors to improve the quality and reliability of Renesas Electronics products, semiconductor products have specific characteristics, such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Unless designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not subject to radiation resistance design. You are responsible for implementing safety measures to guard against the possibility of bodily injury, injury or damage caused by fire, and/or danger to the public in the event of a failure or malfunction of Renesas Electronics products, such as safety design for hardware and software, including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult and impractical, you are responsible for evaluating the safety of the final products or systems manufactured by you.
8. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. You are responsible for carefully and sufficiently investigating applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive, and using Renesas Electronics products in compliance with all these applicable laws and regulations. Renesas Electronics disclaims any and all liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
9. Renesas Electronics products and technologies shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations. You shall comply with any applicable export control laws and regulations promulgated and administered by the governments of any countries asserting jurisdiction over the parties or transactions.
10. It is the responsibility of the buyer or distributor of Renesas Electronics products, or any other party who distributes, disposes of, or otherwise sells or transfers the product to a third party, to notify such third party in advance of the contents and conditions set forth in this document.
11. This document shall not be reprinted, reproduced or duplicated in any form, in whole or in part, without prior written consent of Renesas Electronics.
12. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products.

(Note1) "Renesas Electronics" as used in this document means Renesas Electronics Corporation and also includes its directly or indirectly controlled subsidiaries.

(Note2) "Renesas Electronics product(s)" means any product developed or manufactured by or for Renesas Electronics.

(Rev.4.0-1 November 2017)

## Corporate Headquarters

TOYOSU FORESIA, 3-2-24 Toyosu,  
Koto-ku, Tokyo 135-0061, Japan  
[www.renesas.com](http://www.renesas.com)

## Contact Information

For further information on a product, technology, the most up-to-date version of a document, or your nearest sales office, please visit:  
[www.renesas.com/contact/](http://www.renesas.com/contact/)

## Trademarks

Renesas and the Renesas logo are trademarks of Renesas Electronics Corporation. All trademarks and registered trademarks are the property of their respective owners.