

## Background

As the demand for high-end wireless handsets continues to rise, the ability for OEMs and ODMs to quickly and cost effectively develop new, increasingly advanced models becomes more and more important. Also, it is equally important that these new models take advantage of the performance supported by emerging wireless data standards so that the value of the "killer apps" they bring to the market is fully realized. This application note discusses one solution that addresses these issues and the value that the IDT70P248 Low Power Dual-Port brings to these types of products.

## Dual-Processor Architecture


The high-end, multimedia functions included in today's wireless handsets bring with them more robust processing requirements. As a result, many of the features demanded by consumers out-pace the processing horsepower provided by available baseband processors, including those with integrated ARM cores. In cases such as this, an additional applications processor is required to help off-load some of the processing associated with multimedia applications and the use of a full operating system and application suite.

In addition to the higher level of processing it provides, there are two other benefits of adopting the dual-processor approach shown in Figure 1. First, it is a highly modular architecture that allows a single design to be

used as the basis for numerous models supporting various peripheral, performance and wireless standard requirements. For example, a fixed applications block, with its supporting peripheral components, can be used in conjunction with a variety of different baseband processors, giving OEMs the ability to quickly target multiple geographies using only a limited amount of design resources. Second, this approach relies primarily of off-the-shelf components, which eliminate the need for long and costly ASIC/FPGA development cycles.
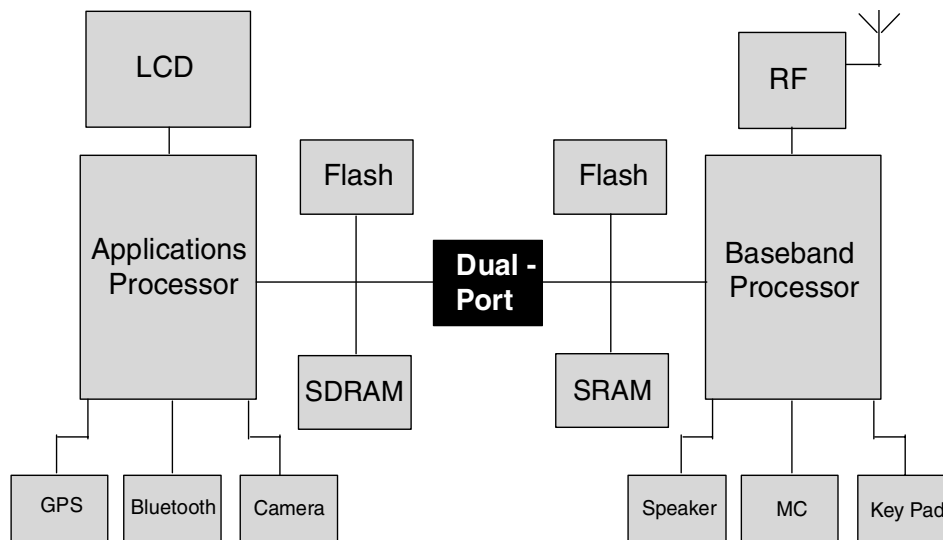
## Inter-processor Communication

Once a dual-processor architecture has been adopted, a means of inter-processor communication must be established so that data can be transferred back and forth from the air I/F and baseband processor to the applications processor. While a number of methods can be employed to facilitate this communication, the IDT70P248 is the only off-the-shelf solution that provides both the bandwidth necessary to support data rates greater than 1Mbps (see Table 1) and the aggressive power and packaging targets demanded by these kinds of applications (see Table 2). Moreover, the Interrupt functionality provided by the IDT70P248 can be used to aid in software flow control and as a polling mechanism to prevent both ports from being simultaneously accessed, keeping the average power consumed to minimum.



6482 drw 01

Figure 1. High-end Wireless Handset

## Low Power Operation

The IDT70P248 has been optimized to consume very little power both when operational and when in standby mode (see Table 3). By supporting ultra-low operating and standby currents and a 1.8V core voltage, the IDT70P248 extends both the talk time and the standby time of the handset by limiting the power drawn from the battery under all conditions.

## Advanced Functionality

In addition to providing high-performance, low-power communication between the two processors, the IDT70P248 also features two specialty functions designed specifically for the wireless handset market. The Input Read Register and Output Drive Register allow both of the processors to monitor and/or drive a number of external binary input devices without sacrificing any additional pins. This increases the overall flexibility of the solution by allowing the limited number of controls pins on the two processors to be used for other purposes.

		UART	USB1.1	Dual-Port
GPRS	171.2 kbps			
cdma2000 1x	307 kbps			
EDGE	384 kbps			
cdma2000 3x	2 Mbps			
W-CDMA	2 Mbps			
cdma2000 1xEV-DO	2.4 Mbps			
cdma2000 1xEV-DV	4.8 Mbps			
WCDMA (HSPDA)	8-10 Mbps			
802.11b	11 Mbps			

6482 tbl01

Table 1. Inter-processor Communication Bandwidth

Symbol	Description	IDT70V24VL	IDT70T24L	IDT70P248	USB 2.0 Host/Controller	USB1.1 Host/Controller
V <sub>DD</sub>	Supply Voltage	3.0	2.5	1.8V	3.3V	3.3V
I <sub>DD</sub>	Operating Current	75mA	50mA	15mA	345mA	50mA
I <sub>SB3</sub>	Standby Current	42uA	25uA	2uA	10.4mA	500uA
P	Operating Power	225mW	125mW	27mW	1.14W	165mW
p	Standby Power	126uW	63uW	4uW	34mW	1.6uW
	Package Size	64mm <sup>2</sup>	64mm <sup>2</sup>	36mm <sup>2</sup>	64mm <sup>2</sup>	100mm <sup>2</sup>

6482 tbl02

Table 2. Package Size and Power Consumption Comparison

Symbol	Parameter	Typ.	Max.	Unit
I <sub>DD</sub>	Dynamic Operating Current (Both Ports Active - CMOS Level Inputs)	15	25	mA
I <sub>SB3</sub>	Standby Current (Both Ports - CMOS Level Inputs)	2	8	uA

Table 3. IDT70P248 Operating and Standby Current Levels <sup>6482 tbi03</sup>

### Input Read Register

The Input Read Register (IRR) of the IDT70P248 captures the status of two external binary input devices connected to the Input Read pins (e.g. DIP switches). This allows either processor to monitor the status of two external devices using only those pins already used to I/F with the IDT70P248. When access to the IRR is enabled, the contents of the IRR are read from the IDT70P248 as a standard memory access to address x0000 from either port and the data is output via the standard I/Os. The IRR supports inputs up to 3.5V ( $V_{IL} \leq 0.4V$ ,  $V_{IH} \geq 1.4V$ ).

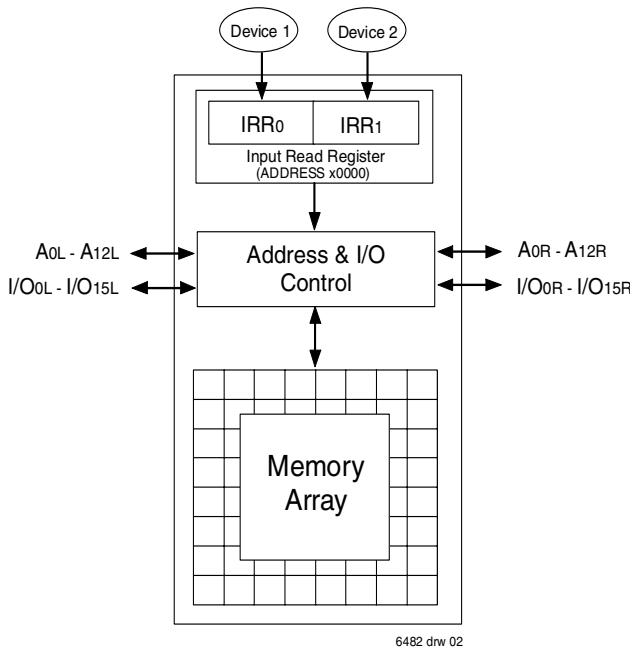


Figure 2. IDT70P248 Input Read Register <sup>6482 drw 02</sup>

### Output Drive Register

The Output Drive Register (ODR) of the IDT70P248 determines the state of up to five external binary-state devices by providing a path to V<sub>ss</sub>

for the external circuit. This gives either processor the ability to control up to five external devices (e.g. LEDs) without sacrificing any additional control signals. The five external devices supported by the ODR can operate at different voltages ( $1.5V \leq V_{SUPPLY} \leq 3.5V$ ), but the combined current of the devices must not exceed 40mA ( $8mA I_{MAX}$  for each external device). When the access to the ODR is enabled, the status of the ODR bits is set using standard write accesses to the IDT70P248 from either port to address x0001 with a "1" corresponding to "on" and a "0" corresponding to "off". The status of the ODR bits can also be read (without changing the status of the bits) via a standard read to address x0001.

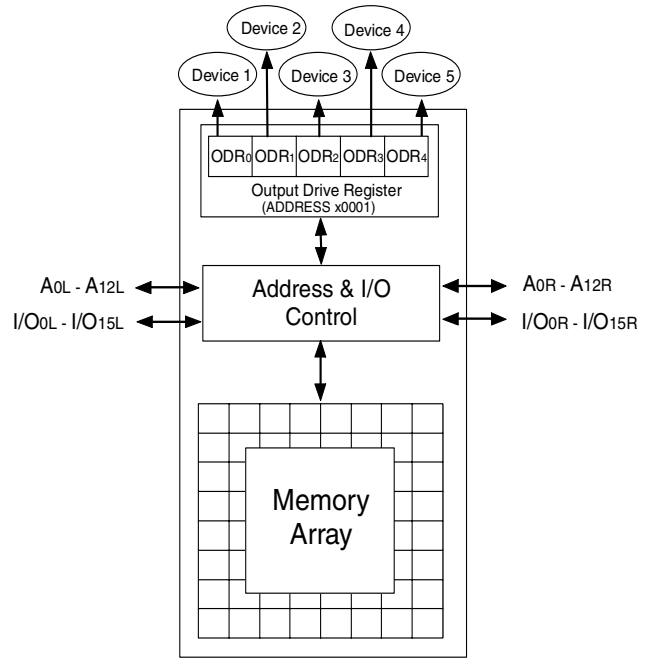


Figure 3. IDT70P248 Output Drive Register <sup>6482 drw 03</sup>

### Summary

As shown here, the dual-processor architecture provides OEMs and ODMs with a powerful, flexible, and cost effective approach to high-end handset designs. Using the IDT70P248 as the communication link between the application and baseband processors further optimizes the performance and power consumption of these designs. By taking advantage of this highly specialized device from IDT, the industry's leading supplier of multi-ports, wireless handset manufacturers can shorten their design cycles while still presenting their customers with a wide array of high performance products.

## Notice

1. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation or any other use of the circuits, software, and information in the design of your product or system. Renesas Electronics disclaims any and all liability for any losses and damages incurred by you or third parties arising from the use of these circuits, software, or information.
2. Renesas Electronics hereby expressly disclaims any warranties against and liability for infringement or any other claims involving patents, copyrights, or other intellectual property rights of third parties, by or arising from the use of Renesas Electronics products or technical information described in this document, including but not limited to, the product data, drawings, charts, programs, algorithms, and application examples.
3. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
4. You shall not alter, modify, copy, or reverse engineer any Renesas Electronics product, whether in whole or in part. Renesas Electronics disclaims any and all liability for any losses or damages incurred by you or third parties arising from such alteration, modification, copying or reverse engineering.
5. Renesas Electronics products are classified according to the following two quality grades: "Standard" and "High Quality". The intended applications for each Renesas Electronics product depends on the product's quality grade, as indicated below.
  - "Standard": Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; industrial robots; etc.
  - "High Quality": Transportation equipment (automobiles, trains, ships, etc.); traffic control (traffic lights); large-scale communication equipment; key financial terminal systems; safety control equipment; etc.Unless expressly designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not intended or authorized for use in products or systems that may pose a direct threat to human life or bodily injury (artificial life support devices or systems; surgical implantations; etc.), or may cause serious property damage (space system; undersea repeaters; nuclear power control systems; aircraft control systems; key plant systems; military equipment; etc.). Renesas Electronics disclaims any and all liability for any damages or losses incurred by you or any third parties arising from the use of any Renesas Electronics product that is inconsistent with any Renesas Electronics data sheet, user's manual or other Renesas Electronics document.
6. When using Renesas Electronics products, refer to the latest product information (data sheets, user's manuals, application notes, "General Notes for Handling and Using Semiconductor Devices" in the reliability handbook, etc.), and ensure that usage conditions are within the ranges specified by Renesas Electronics with respect to maximum ratings, operating power supply voltage range, heat dissipation characteristics, installation, etc. Renesas Electronics disclaims any and all liability for any malfunctions, failure or accident arising out of the use of Renesas Electronics products outside of such specified ranges.
7. Although Renesas Electronics endeavors to improve the quality and reliability of Renesas Electronics products, semiconductor products have specific characteristics, such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Unless designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not subject to radiation resistance design. You are responsible for implementing safety measures to guard against the possibility of bodily injury, injury or damage caused by fire, and/or danger to the public in the event of a failure or malfunction of Renesas Electronics products, such as safety design for hardware and software, including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult and impractical, you are responsible for evaluating the safety of the final products or systems manufactured by you.
8. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. You are responsible for carefully and sufficiently investigating applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive, and using Renesas Electronics products in compliance with all these applicable laws and regulations. Renesas Electronics disclaims any and all liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
9. Renesas Electronics products and technologies shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations. You shall comply with any applicable export control laws and regulations promulgated and administered by the governments of any countries asserting jurisdiction over the parties or transactions.
10. It is the responsibility of the buyer or distributor of Renesas Electronics products, or any other party who distributes, disposes of, or otherwise sells or transfers the product to a third party, to notify such third party in advance of the contents and conditions set forth in this document.
11. This document shall not be reprinted, reproduced or duplicated in any form, in whole or in part, without prior written consent of Renesas Electronics.
12. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products.

(Note1) "Renesas Electronics" as used in this document means Renesas Electronics Corporation and also includes its directly or indirectly controlled subsidiaries.

(Note2) "Renesas Electronics product(s)" means any product developed or manufactured by or for Renesas Electronics.

(Rev.4.0-1 November 2017)

## Corporate Headquarters

TOYOSU FORESIA, 3-2-24 Toyosu,  
Koto-ku, Tokyo 135-0061, Japan  
[www.renesas.com](http://www.renesas.com)

## Contact Information

For further information on a product, technology, the most up-to-date version of a document, or your nearest sales office, please visit:  
[www.renesas.com/contact/](http://www.renesas.com/contact/)

## Trademarks

Renesas and the Renesas logo are trademarks of Renesas Electronics Corporation. All trademarks and registered trademarks are the property of their respective owners.